

$$G_{out} = \frac{A_{open}}{1 + \frac{R_o}{R_s}} = \frac{A_{open}}{1 + \frac{1}{\omega_n^2 C_s}} = \frac{A_{open}}{1 + \frac{1}{\omega_n^2 R_s C_s}}$$

Electronics (Section (5))

To have analog circuit design
We should know

- Bandwidth (closed loop) \rightarrow Gain bandwidth (open loop)

- Gain

- Slew rate

- O/p swing (Range of o/p voltage at which all transistors are still operating in sat.)
 \rightarrow linearly

- Noise & offset

* How we calculate these parameters using audience &
What are parameters controlling them?

(a) DC gain / GBW / PSRR / Stability {AC analysis}

G_m^{op} \downarrow \downarrow $G_m^{op}/load$ \downarrow poles we use from
o/p impedance (R_o) capacitance path from i/p
to o/p as well as zeros due to multipath

(b) Stability [Open loop + CMFB] {Stb analysis}

We need to have $PH > 45^\circ$ (M^-) to have stable system

To get such PM or even $PM \approx 60$.

For dominant pole system

$$A(s) = \frac{A_0}{(1 + \frac{s}{\omega_B})(1 + \frac{s}{\omega_{P_2}})}$$

↓
dominant
pole

We should have $[\omega_{P_2} = 2^* GBW]$

$$[\omega_{P_2} = 2^* \frac{9mH}{C_L}] \text{ to get } (PM=60)$$

which is my optimum value


(c) Noise

{noise analysis}

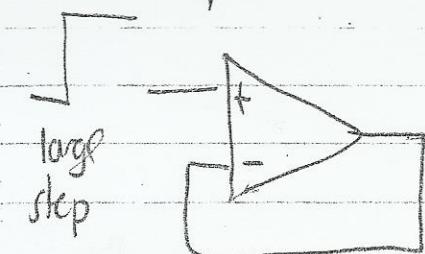(d) Slew rate, o/p swing

{transient analysis}

↳ to see when clipping occurs to
the o/p signal



$$\left| \frac{dV_{out}}{dt} \right|_{max} = \text{Slew rate}$$


(e) Offset

{Monte carlo simulation}

* If we consider the op-amp as 2 part network, have

$V_{ICM} = 0$ bias transistors to work properly

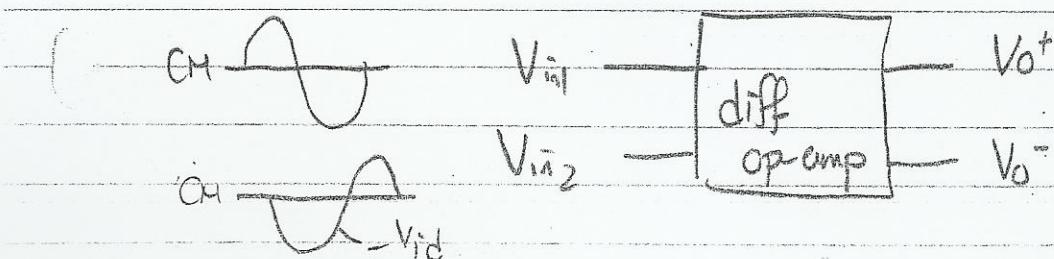$V_{IDM} = \text{Signal to be amplified}$
(Small signal)



$$\therefore V_{id} = V_{in1} - V_{in2}$$

$$\therefore V_{if} = V_{cm} + \frac{V_{id}}{2}$$

$$V_{cm} = \frac{V_{in1} + V_{in2}}{2}$$

$$V_{in2} = V_{cm} - \frac{V_{id}}{2}$$

So now, we've got the op as well (CM) & diff mode

$$\begin{bmatrix} V_{od} \\ V_{ocm} \end{bmatrix} = \begin{bmatrix} A_{dd} & A_{cd} \\ A_{cd} & A_{cc} \end{bmatrix} \begin{bmatrix} V_{id} \\ V_{lcm} \end{bmatrix}$$

$$\therefore V_{od} = \underbrace{A_{dd} V_{id}}_{\text{DC gain}} + \underbrace{A_{cd} V_{lcm}}_{\text{AC gain}}$$

we don't need to have (CM) sig contribution in the diff. op.

So that's why we need to see $(CMRR) = \left| \frac{A_{dd}}{A_{cd}} \right|$

to be as large as possible

⇒ So first use (I_D) & (V_{ce}) to operate the transistors in saturation,
& after that use small signal i/p to be amplified using DC gain

⇒ What does gain $(A(s))$ & GBW & Slew rate represent?


(a) Gain $A(s) \Rightarrow$ Accuracy of op-amp.

for finite gain (A_0) :

$$\text{so } A(s) = A_0$$

$$\text{Ideal gain} = 1 + \frac{R_2}{R_1} = \frac{1}{B}$$
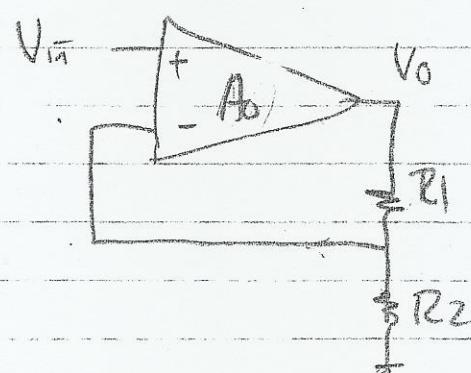
$$\left(B = \frac{R_2}{R_1 + R_2} \right) \Rightarrow$$



$$\text{Real gain} = \frac{A_0}{1 + A_0 B} = \frac{1}{\frac{1}{B} + B} = \frac{B}{1 + \frac{1}{B}}$$


$$= \frac{1}{B(1 + \frac{1}{A_0 B})} \quad \text{using binomial theorem}$$

$$= \frac{1}{B} \left(1 - \frac{1}{A_0 B} \right)$$

∴ Gain error = $\frac{1}{A_0 B}$

So if it's required to be 0.1%
for best (B) case = 1

buffer connected

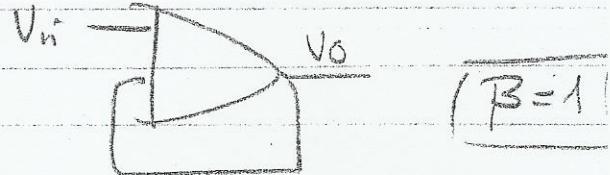


∴ $A_0 = 100e = 60 \text{ dB}$

So it decides the gain error (Accuracy of sys)

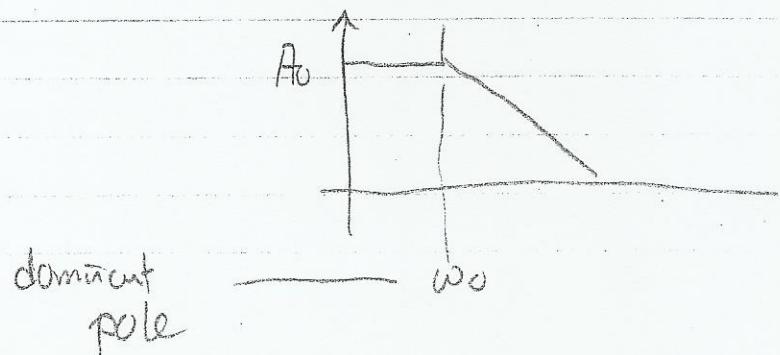(b) Gain-bandwidth (GBW)

$$= \text{Gain} * \text{BW}$$

For single pole op-amp. $\text{BW} = \omega_0 = \frac{1}{R_{\text{out}} * C}$



$$GBW = G_m * R_{out} + \frac{1}{R_{out} * C_L} = A_o \omega_d$$

$$GBW = \frac{G_m}{C_L} = \frac{G_m / i/p}{C_L}$$

it represents speed of the op-amp


Why?

for single pole op-amp

$$A(s) = \frac{R_o}{1 + \frac{s}{\omega_p}} \quad \omega_p = \frac{1}{R_{out} * C_L}$$

$$A(s) \approx \frac{A_o \omega_d}{s} = \frac{GBW}{s}$$

for the same config

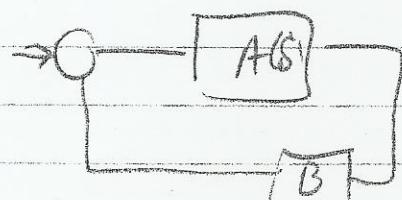


$$\frac{V_o(s)}{V_{in}} = \frac{A(s)}{1 + A(s)\beta}$$

$$\frac{V_o(s)}{V_{in}} = \frac{GBW}{s + GBW * \beta} \quad \left\{ \text{d-1} \right\}$$

$$\frac{V_o(t)}{V_{in}} = (1 - e^{-t/\tau})$$

$$\tau = \frac{1}{\beta * GBW}$$

So that if small clk i/p.

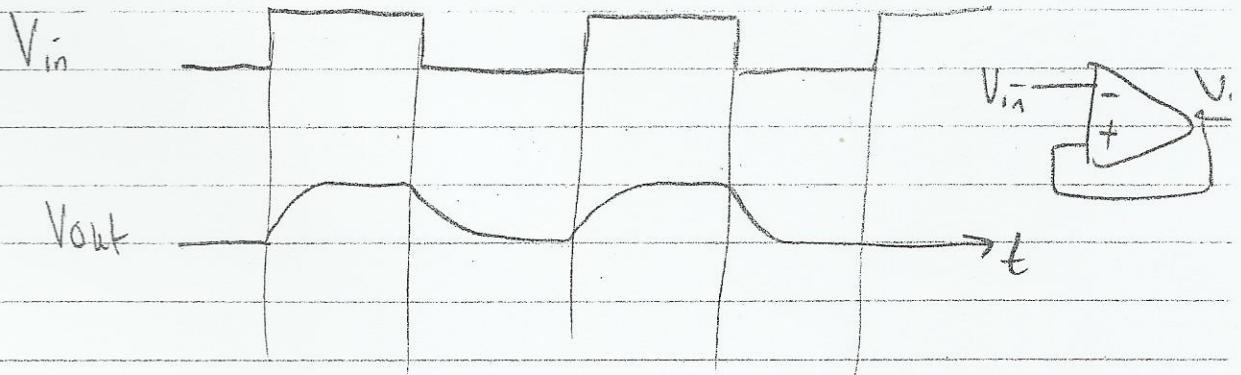


So that is why (GBW) represent speed of my system

It decides the speed at which the o/p will respond to the input

(C) Slew rate

Instead of applying small clock i/p
Apply

Large unit step $[0 - V_{DD}]$

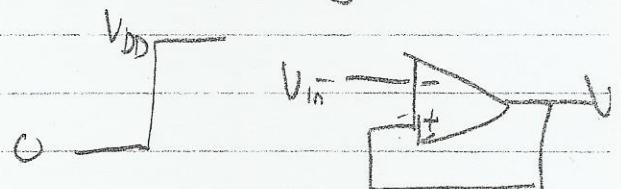

Slew rate represents

V_{out}

t_{12}


$$\left. \frac{dV_{out}}{dt} \right|_{max} = \text{Slew rate} = \frac{I_{ss}}{C_L}$$

as it will steer all the current in one branch

& that current would charge the capacitors at the load


$$\text{so } I = C \frac{dV_{out}}{dt}$$

$$\text{so } \left| \frac{dV_{out}}{dt} \right|_{\text{max}} = \frac{I_{SS}}{C}$$

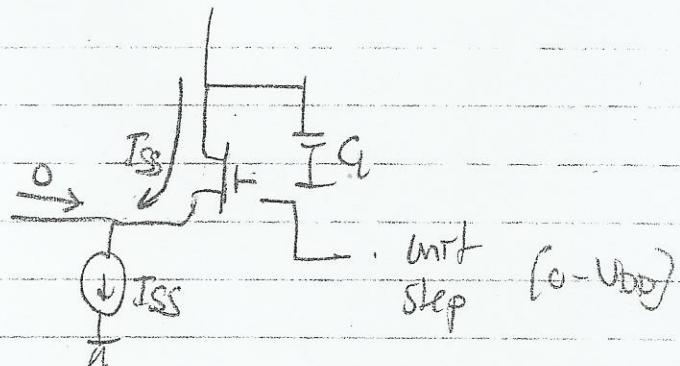

* Fully differential Vs. Single ended

→ for fully diff. configuration

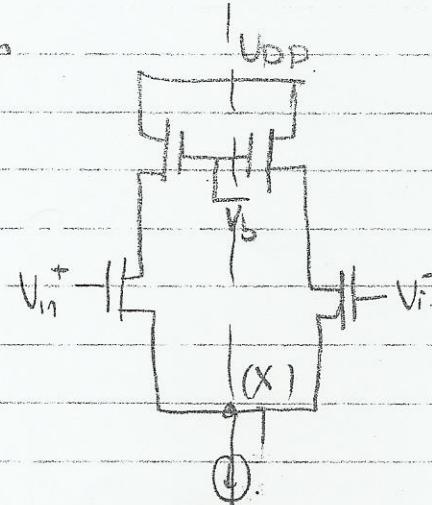

line of symmetry

When we solve for


(a) Differential inputs $\left(\frac{V_{in+}}{2}, -\frac{V_{in-}}{2} \right)$

We've node (x) as virtual gnd

this source

follower node

so this virtual ground

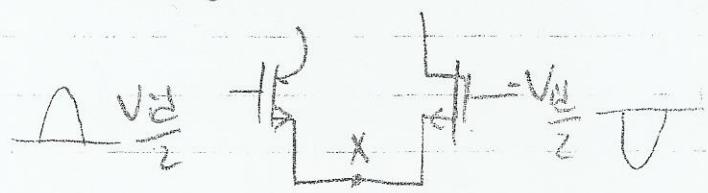

So that all points on line of symmetry are virtual ground {for AC analysis}

(b) Common mode input

Now line of symmetry, will divide resistances
(seen at node X) into (2) parallel resistors

& the points on line of symmetry are open circuits

→ For single ended


No half model can be used

So we must solve for the whole circuit

To find

$R_{out} =$

from the basic principles

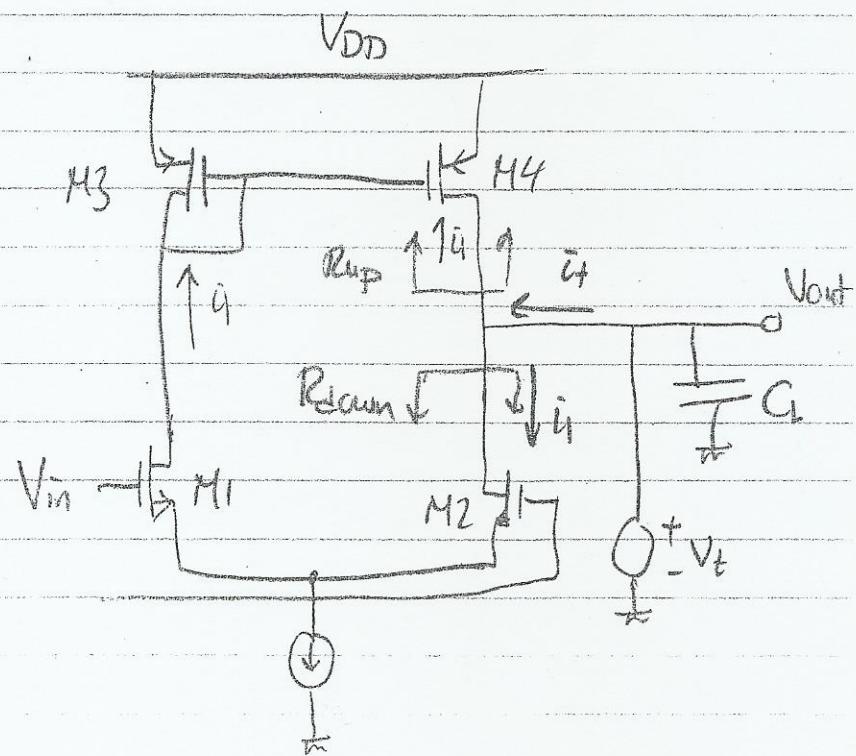

$$I_{in} \bar{V}_t = \frac{V_t}{R_{in}} + i_1 + i_2 \quad (\text{KCL at o/p node})$$

$$\text{so } R_{\text{out}} = r_{\text{op}} \parallel \frac{R_{\text{down}}}{2}$$

$$R_{\text{down}} = r_{\text{on}} (1 + g_m R_{S_2})$$


$$R_{S_2} \approx \frac{1}{g_m}$$

$$R_{\text{down}} = r_{\text{on}} (1 + g_{m_2}/g_{m_1}) \approx 2r_{\text{on}}$$

$$\text{so } R_{\text{out}} = r_{\text{op}} \parallel \frac{2r_{\text{on}}}{2} \approx r_{\text{op}} \parallel r_{\text{on}}$$

$$\text{so } A_{\text{diff}} = g_m (r_{\text{op}} \parallel r_{\text{on}})$$

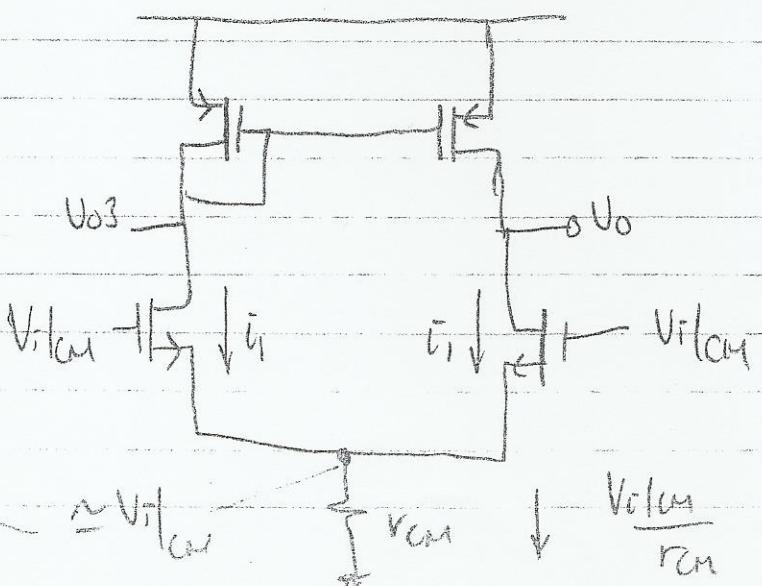\Rightarrow What about calculating A_{dc} for the same circuit?



Source
follower


From symmetry $V_{03} \approx V_{0CM}$

$$V_{03} = i_1 * R_{int} \Big|_{V_{03}}$$

$$R_{int} = \frac{L}{g_{mp}}$$

$$= -\frac{i_1}{g_{mp}}$$

$$i_1 = \frac{V_{1CM}}{2r_{cm}}$$

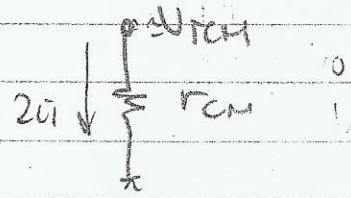

$$V_{03} = \frac{V_{1CM}}{2r_{cm} g_{mp}} = V_{0CM}$$

$$CM_{go} = \frac{1}{2r_{cm} g_{mp}}$$

$$* CMRR = \left| \frac{A_{CM}}{A_{AC}} \right| = g_{mn} (\text{ron} // \text{rop}) (2r_{cm} g_m)$$

→ How to get conditions on biasing voltages in fully differential configuration?

- * Put one condition on transistor to be in saturation

$$V_{GD} < V_{th}$$

$$V_b - V_{th}$$

(That will get upper bound in NMOS


& lower bound in PMOS)

- * To move from (V_b) to the gnd direction
& get conditions to be in sat. ($V_{DS} = V_{eff}$)
& ($V_{GS} = V_{eff} + V_{th}$)




Problem Set II

Problem (1)

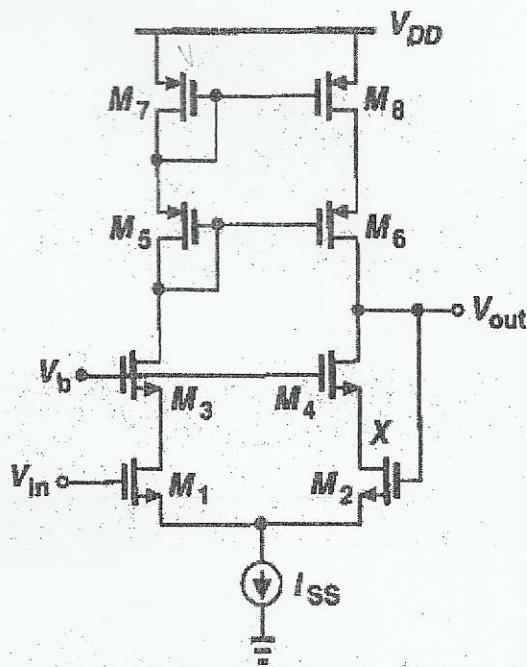

For the previous circuit, find the region of operation of each transistor while varying the input V_{in} from 0 to V_{DD} . Find the output range for proper operation (V_{out} tracks V_{in}).


Problem (2)

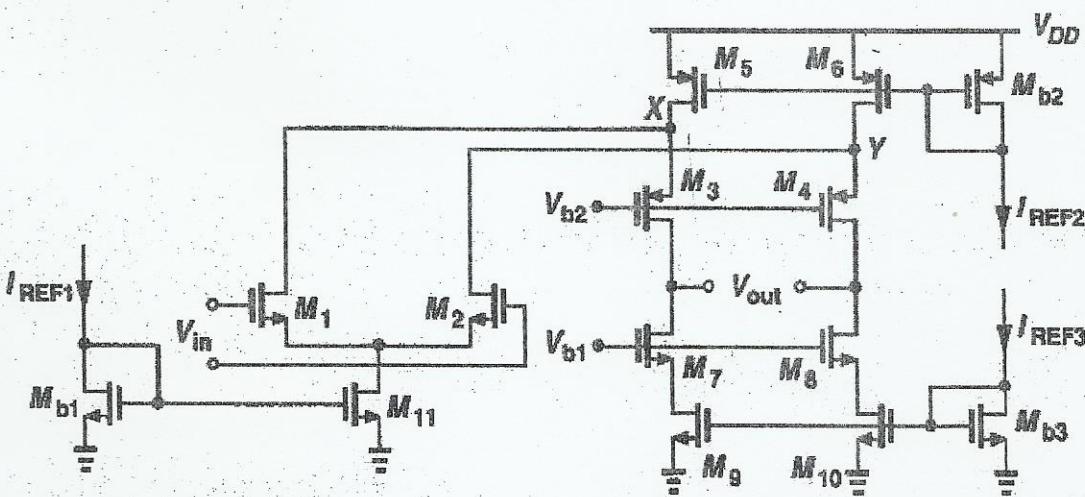

For the previous circuit:

- 1- Find the relation between I_{REF1} , I_{REF2} and I_{REF3} .
- 2- Assume output load capacitance C_L at V_{out} , find the exact expression of the Gain-Bandwidth product (GBW) in terms of the circuit parameters.
- 3- Find the maximum output range as a function of V_{b1} and V_{b2} .
- 4- Find the values of V_{b1} and V_{b2} for maximum output swing.

Problem (3)

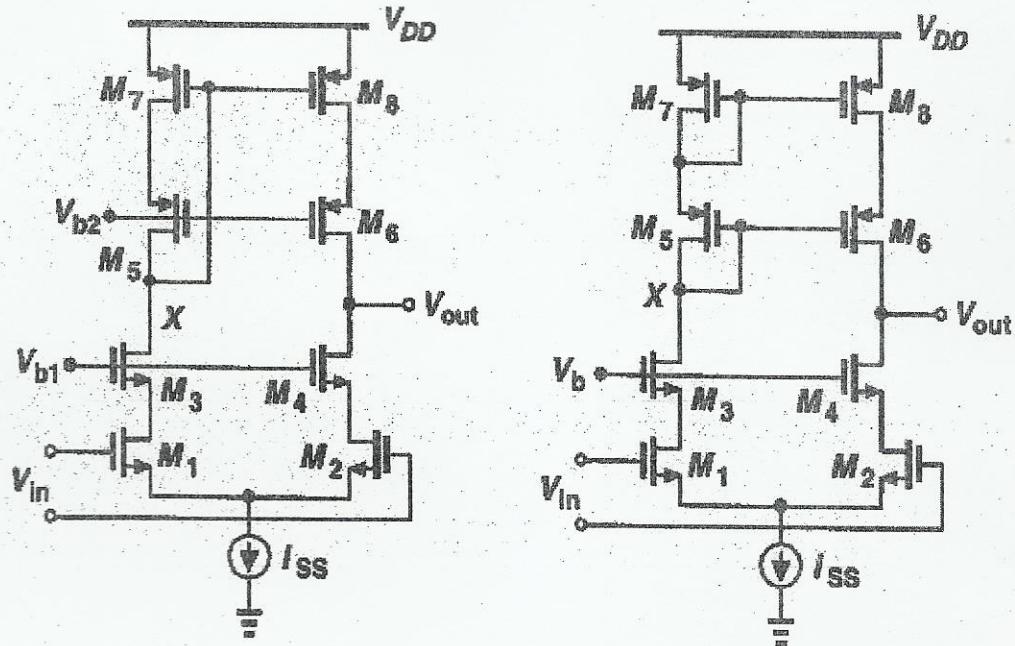

Compare between the two circuits in terms of:

- 1- DC-gain
- 2- GBW (assume a load capacitance C_L)
- 3- Maximum available output swing.

Problem (3)




Find the R_{out} of the first circuit and hence find the G_m and A_v of the second circuit.

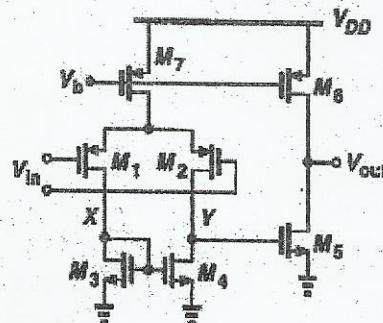Problem (4)


For the two-stage opamp below, $V_{DD} = 2.5V$, $\mu_n C_{ox} = 100 \mu A/V$, $\mu_p C_{ox} = 50 \mu A/V$ and for a total power consumption of 6mW, find the maximum GBW for a load capacitance of $C_L = 1pF$ and such that the non-dominant pole is double the GBW product. For this value, find the DC-gain and the maximum output swing.

Assume: $V_{OD5}=V_{OD6}$ and $V_{OD1}=V_{OD3}$.



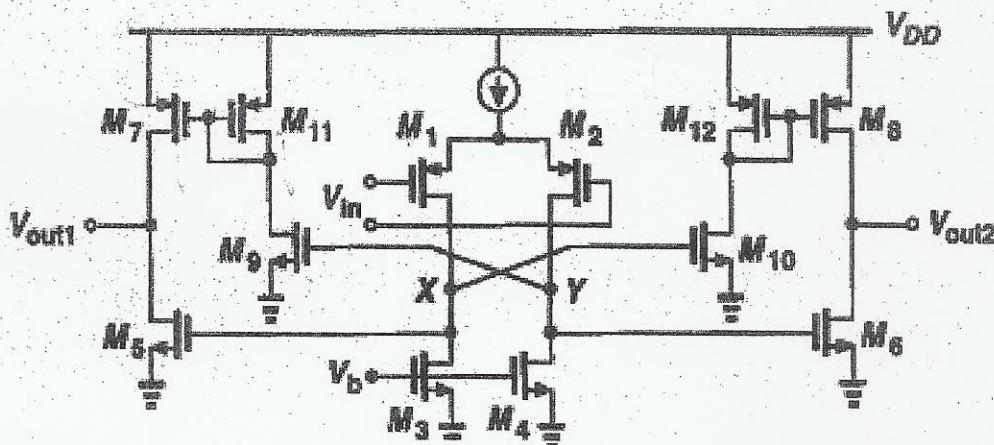Problem (5)

Find the DC-gain of the following opamp circuit.



W + R Circuits Section [1]

Classical Electronics + Electronics Sights
Sheet [2] outfit/p

Problem 1)

For M1

$$V_{in} > V_{eff_1} + V_{th_1} + V_{eff_{ss}}$$

$$V_{GD_1} < V_{th_1}$$

$$V_{in} - (V_b - V_{eff_3} - V_{th_3}) < V_{th_1}$$

$$V_{in} < V_b - V_{eff_3} + V_{th_1} - V_{th_3}$$

for M3

$$V_{GD_3} < V_{th_3}$$

$$V_b < V_{th_3} + V_{DD} - [V_{eff_2} + (V_{th_2}) + V_{eff_5} + (V_{th_5})]$$

for M2

$$V_{GD_2} < V_{th_2}$$

$$V_{out} < V_{th_2} + V_b - (V_{eff_4} + V_{th_4})$$

for M₄

(2)

$$V_{GD_4} < V_{th_4}$$

$$V_b - V_{out} < V_{th_4}$$

$$- V_{out} < V_{th_4} - V_b$$

$$\boxed{V_{out} > V_b - V_{th_4}}$$

$$\Rightarrow \boxed{V_{out} > (V_{in} - V_{eff\ 3} + V_{th} - V_{th\ 4})}$$


for M₆

$$V_{DG_6} < |V_{th_6}|$$


$$\boxed{V_{out} < V_{DD} - [V_{eff\ 2} + |V_{th\ 2}| + V_{eff\ 5} + |V_{th\ 5}|]}$$

Problem [2]

[3]

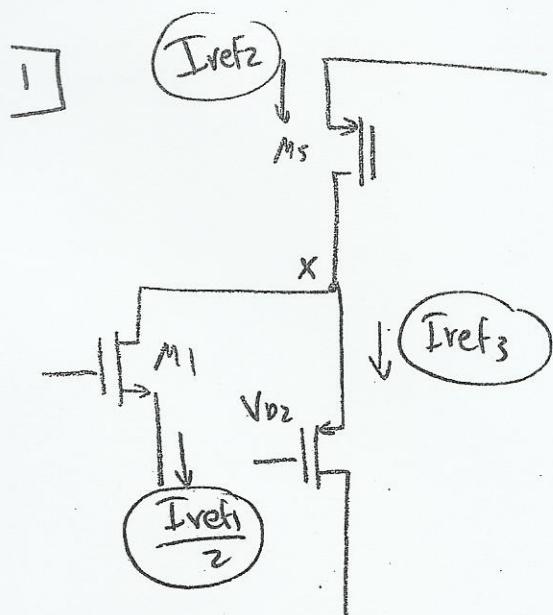

2] to get G_m

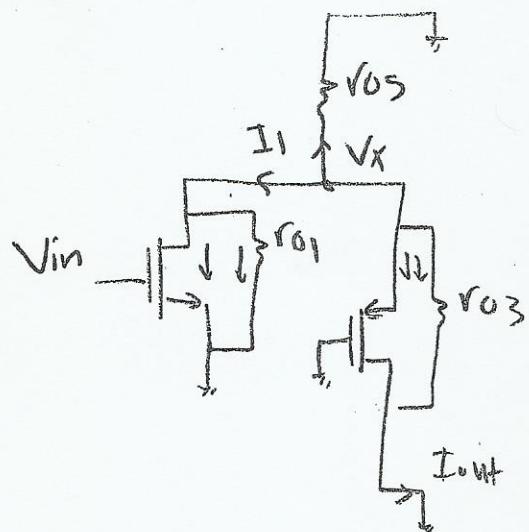

$$I_1 = g_m V_{in} + \frac{V_x}{r_{01}}$$

KCL at V_x

$$I_1 + \frac{V_x}{r_{05}} + I_{out} = 0$$

$$I_{out} = -g_m V_{in} - \frac{V_x}{r_{01}} - \frac{V_x}{r_{05}} \rightarrow (1)$$

$$V_x = r_{o3} (I_{out} - g_{m3} V_x) \quad (4)$$

$$V_x (1 + g_{m3} r_{o3}) = r_{o3} I_{out}$$

$$\boxed{V_x = \frac{r_{o3}}{1 + g_{m3} r_{o3}} I_{out}}$$

then in (1)

$$I_{out} = -g_{m1} V_{in} - \left(\frac{1}{r_{o1}} + \frac{1}{r_{o5}} \right) \left(\frac{r_{o3}}{1 + g_{m3} r_{o3}} \right) I_{out}$$

$$I_{out} \left[1 + \left(\frac{1}{r_{o1}} + \frac{1}{r_{o5}} \right) \left(\frac{r_{o3}}{1 + g_{m3} r_{o3}} \right) \right] = -g_{m1} V_i$$

then

$$\boxed{G_m = \frac{I_{out}}{V_{in}} = \frac{-g_{m1}}{1 + \left(\frac{1}{r_{o1}} + \frac{1}{r_{o5}} \right) \left(\frac{r_{o3}}{1 + g_{m3} r_{o3}} \right)}}$$

then $A_V = -G_m R_{out}$ (gain of half circuit)

$$A_d \text{ (diff. gain)} = -A_V = -G_m R_{out}$$

$$\text{Dominant pole} = \omega_d = \frac{1}{C_L R_{out}}$$

$$\text{then } GBW = A_d \omega_d = -G_m R_{out} \frac{1}{C_L R_{out}} = \frac{g_{m1}}{C_L \left[1 + \left(\frac{1}{r_{o1}} + \frac{1}{r_{o5}} \right) \left(\frac{r_{o3}}{1 + g_{m3} r_{o3}} \right) \right]}$$

$$\boxed{GBW = \frac{g_{m1}}{C_L \left[1 + \left(\frac{1}{r_{o1}} + \frac{1}{r_{o5}} \right) \sqrt{\frac{r_{o3}}{1 + g_{m3} r_{o3}}} \right]} \quad \square}$$

[3]

for M_3

$$V_{DG_3} < V_{th_3}$$

$$V_{out} < |V_{th_3}| + V_{b_2}$$

[5]

$$V_{out\ max} = |V_{th_3}| + V_{b_2\ max}$$

for M_7

$$V_{GD_7} < V_{th_7}$$

$$V_{b_1} < V_{th_7} + V_{out}$$

$$V_{out} > V_{b_1} - V_{th_7}$$

$$V_{out\ min} = V_{b_1\ min} - V_{th_7}$$

Maximum output swing for half circuit

$$= [|V_{th_3}| + V_{b_2\ max} - V_{b_1\ min} + V_{th_7}]$$

Maximum output swing for differential circuit

$$= 2 \times [|V_{th_3}| + V_{b_2\ max} - V_{b_1\ min} + V_{th_7}]$$

[4]


For maximum output swing

$$V_{b_1} \text{ should be min.} = V_{eff_2} + V_{th_2} + V_{eff_3}$$

$$V_{b_2} \text{ should be max.} = V_{DD} - V_{eff_5} - [V_{eff_3} + V_{th_4}]$$

Problem 3

(6)

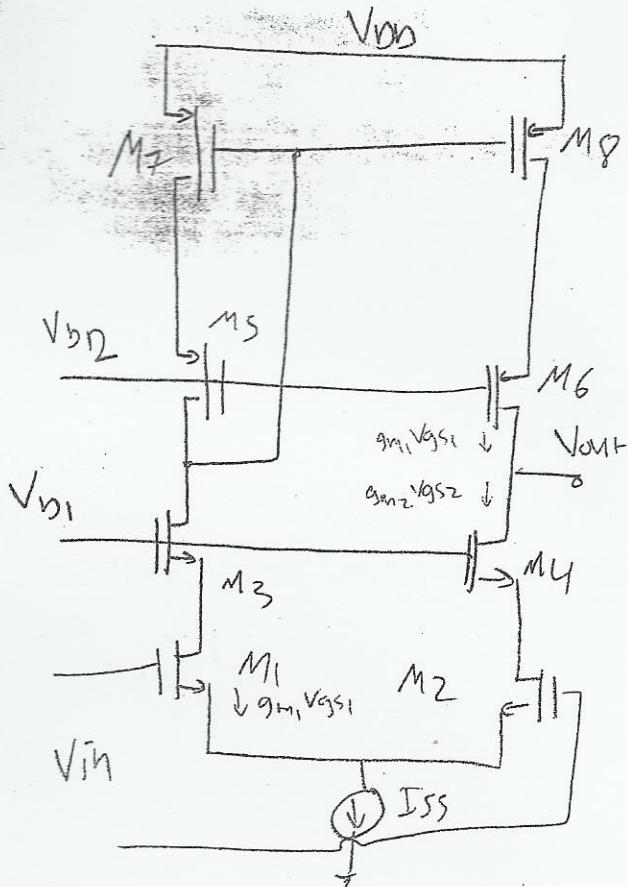

① DC gain

$$G_m = g_{m_1}$$


$$R_{out} \approx g_{m_4} r_{o_4} / r_{o_2} \parallel g_{m_6} r_{o_6} / r_{o_8}$$

$$A_V = G_m R_{out}$$

② GBW

$$W_d = \frac{1}{R_{out} C_L}$$
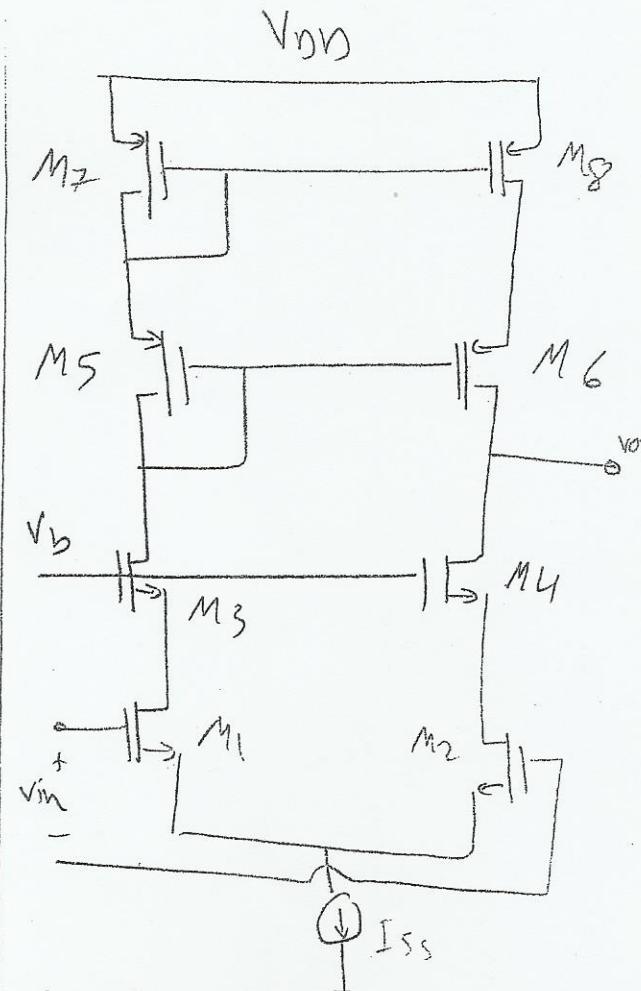
$$GBW = A_V W_d = \frac{G_m R_{out}}{R_{out} + C_L} = \frac{g_{m_1}}{C_L}$$



① DC gain

$$G_m = g_{m_1}$$

$$R_{out} \approx g_{m_4} r_{o_4} / r_{o_2} \parallel g_{m_6} r_{o_6} / r_{o_8}$$

$$A_V = G_m R_{out}$$

② GBW

$$W_d = \frac{1}{R_{out} C_L}$$

$$GBW = A_V W_d = \frac{G_m R_{out}}{R_{out} + C_L} = \frac{g_{m_1}}{C_L}$$

③ Maximum output swing

$$V_{out\ min} = V_{eff4} + V_{eff2} + V_{effss}$$

for M6

$$-V_{b2} + V_{out} < |V_{thd}|$$

$$|V_{out}| < |V_{thd}| + V_{b2}$$

for M5

$$V_{b6} < |V_{th5}|$$

No -

$$V_{eff2} + |V_{th7}| < V_{b2} + |V_{th5}|$$

for getting
minimum V_{b2}

but we need max V_{b2}

for M7

$$V_{b7} < |V_{th7}|$$

$$\begin{aligned} V_{b2} - [V_{eff5} + |V_{th5}|] \\ - (V_{bb} - [V_{eff7} + |V_{th7}|]) < V_{th7} \end{aligned}$$

$$V_{b2} < V_{bb} - V_{eff7} + V_{eff5} + |V_{th5}|$$

then $V_{out\ max} < |V_{th6}| + V_{b\ max}$

$$\begin{aligned} V_{out\ max} = |V_{th6}| + V_{bb} - V_{eff7} \\ + V_{eff5} + |V_{th5}| \end{aligned}$$

swing = $V_{out\ max} - V_{out\ min}$

③ Max. output swing

$$V_{out\ min} = V_{eff4} + V_{eff2} + V_{effss}$$

for M6

$$V_{b6} < |V_{th6}|$$

$$|V_{out}| < |V_{th6}| + V_{bb} - [V_{eff7} + |V_{th7}| \\ + V_{eff5} + |V_{th5}|]$$


$$V_{out\ max} = |V_{th6}| + V_{bb} - [V_{eff7} \\ + V_{eff5} + |V_{th5}|]$$

$$\text{Max. swing} = V_{out\ max} - V_{out\ min}$$

Problem (4)

(8)

1st Circuit

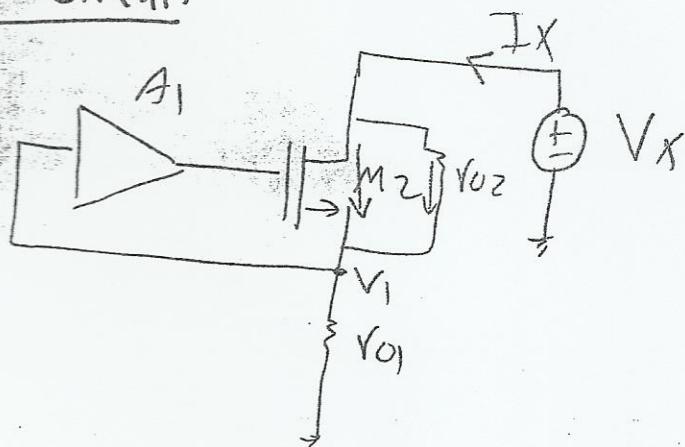

$$I_x = g_m V_{gs} + \frac{V_x - V_1}{R_{02}}$$

$$V_{gs} = A_1 V_1 - V_1 = (A_1 - 1) V_1$$

$$g_m V_1 = I_x R_{01}$$

$$\text{then } V_{gs} = (A_1 - 1) (I_x R_{01})$$


$$I_x = g_m (A_1 - 1) (I_x R_{01}) + \left(\frac{V_x - I_x R_{01}}{R_{02}} \right)$$

$$I_x [R_{02} - g_m (A_1 - 1) R_{01} R_{02} + R_{01}] = V_x$$


$$R_{out} = \frac{V_x}{I_x} = (R_{01} + R_{02}) - g_m (A_1 - 1) R_{01} R_{02}$$

For the 2nd Circuit

(9)

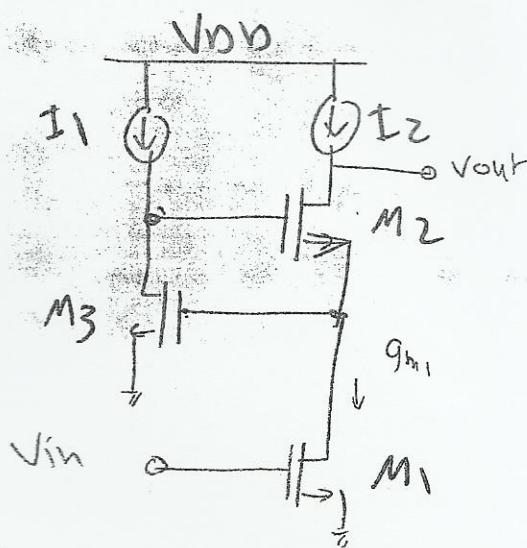

To get G_m

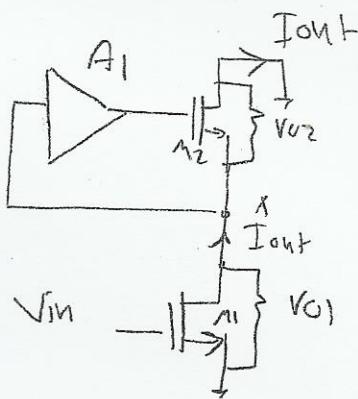

$$I_{out} = - \left[g_{m_2} V_{gs_2} + \frac{0 - V_x}{r_{o2}} \right]$$

$$I_{out} = \frac{V_x}{r_{o2}} - g_{m_2} (A_1 - 1) V_x$$

$$V_x = (-I_{out} - g_{m_1} V_{in}) V_{o1}$$

then $I_{out} = \left[\frac{1}{r_{o2}} - g_{m_2} (A_1 - 1) \right] V_{o1} [-I_{out} - g_{m_1} V_{in}]$

$$I_{out} [1 + B V_{o1}] = B V_{o1} (-g_{m_1} V_{in})$$


$$G_m = \frac{I_{out}}{V_{in}} = \frac{-B V_{o1} g_{m_1}}{1 + B V_{o1}} \approx -g_{m_1}$$

$$\text{Where } B = \frac{1}{r_{o2}} - g_{m_2} (A_1 - 1)$$

To get R_{out}

[10]

$$V_{in} = 0$$
$$V_{GS1} = 0$$

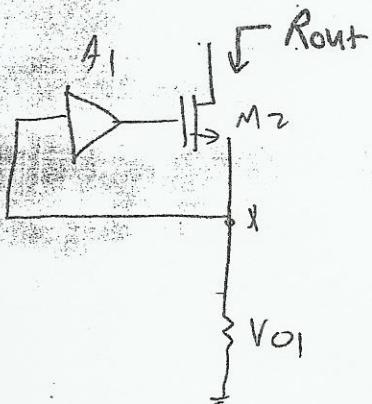


R_{out} (from the 1st circuit)

$$= (V_{G1} + r_{02}) - g_m (A_1 - 1) r_{01} r_{02}$$

then
$$Av = g_m R_{out}$$

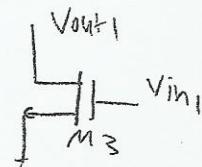Where
$$A_1 = -g_m r_{03}$$
 → Common source amplifier



Problem (5)

(11)

Given :- $V_{DD} = 2.5V$

$$M_n C_{ox} = 100 \text{ mA/V}$$

$$M_P C_{ox} = 50 \text{ mA/V}$$

$$P = 6 \text{ mW}$$

$$C_y = 1 \text{ pF}$$

$$C_L = 1 \text{ pF}$$

$$W_{nd} = 2 \text{ GBW}$$

$$V_{DD_5} = V_{DD_6}$$

$$V_{DD_1} = V_{DD_3}$$

$$(r_o) = \frac{6000L}{I} \rightarrow \begin{array}{l} \text{in } M\Omega \\ \text{in mA} \end{array}$$

$$V_{thn} = 0.5V$$

$$V_{thp} = -0.5V$$

Soln

1st stage :-

$$G_{m_I} \approx -g_{m_1}$$

$$R_{out_I} \approx r_{oy} // r_{o2} \approx \frac{r_{oy}}{2}$$

2nd stage

$$G_{m_{II}} \approx -g_{m_5}$$

$$R_{out_{II}} \approx r_{o5} // r_{o6} \approx \frac{r_{o5}}{2}$$

$$\text{Gain} = A_{V_I} * A_{V_{II}}$$

$$W_d = \frac{1}{C_L R_{out_{II}}}$$

$$W_{nd} = \frac{1}{C_y R_{out_I}}$$

[12]

$$\text{Power} = 6\text{mW}$$

$$(I_7 + I_6) V_{DD} = 6\text{mW}$$

$$(I_7 + I_6) = 2.4\text{ mA}$$

$$2I_1 + I_6 = 2.4\text{ mA}$$

let $V_{OD5} = V_{OD6} = V_{OD7} = 0.2\text{ V}$

$$V_{OD1} = V_{OD3} = V_{OD2} = V_{OD4} = 0.15\text{ V}$$

let $I_6 = 60\text{ mA} = 0.1\text{ mA}$

then $I_1 = I_2 = \frac{I_7}{2} = 1.15\text{ mA}$

$$\text{then } g_{m1} = \frac{2I_1}{V_{OD1}} = \frac{46}{3}\text{ mA/V}$$

$$g_{m5} = \frac{2I_5}{V_{OD5}} = 1\text{ mA/V}$$

$$R_{out\ I} = \frac{3000 L_4}{1.15}$$

$$R_{out\ II} = \frac{3000 L_5}{0.1}$$

then $W_{nd} = \frac{23 \times 10''}{6 L_4}$

$$W_d = \frac{10^8}{3 L_5}$$

$$\text{Gain} = \frac{g_m}{g_{m5}} \frac{R_{out\ I}}{R_{out\ II}}$$

[13]

$$= (1) \left(\frac{46}{3}\right) (10^{-6}) \left(\frac{6000 L_4}{2 \times 1.15}\right) \left(\frac{6000 L_5}{2 \times 0.1}\right)$$

$$\boxed{\text{Gain} = 1200 L_4 L_5}$$

$$\text{for } W_{nd} = 26 \text{ BW} = 2 * \text{Gain} * W_d$$

$$\frac{23 \times 10^{11}}{6.5 L_4} = 2 (1200) (L_4 L_5) \left(\frac{10^8}{3 L_5}\right)$$

$$\text{then } L_4 = \sqrt{\frac{115}{24}} \simeq 2.18898 \text{ Mm}$$

$$\text{let } L_2 = L_4$$

$$\text{let } L_5 = L_6 = 5 \text{ Mm}$$

$$\text{then } \boxed{W_d = \frac{20}{3} \times 10^6 \text{ rad/sec}}$$

$$\boxed{W_{nd} = 1.75119 \times 10^{11} \text{ rad/sec}}$$

$$\boxed{\text{Gain} = 13133.925 \text{ V/V}}$$

14

for M₅

$$I_5 = \frac{V_{DD}}{2} V_{DD5}^2$$

$$100 = (0.5)(100) \frac{W}{L} \Big|_5 (0.2)^2$$

$$\boxed{W_5 = 50 L_5}$$

for M₆

$$I_6 = \frac{V_{DD}}{2} V_{DD6}^2$$

$$100 = (0.5)(50) \frac{W}{L} \Big|_6 (0.2)^2$$

$$\boxed{W_6 = 100 L_6}$$

for M₂

$$\boxed{W_2 = 2044.44 L_2}$$

for M₄

$$\boxed{W_4 = 1022.2 L_4}$$

$$\text{output swing} = V_{out\max} - V_{out\min}$$

$$= (V_{DD} - V_{eff6}) - (V_{eff5})$$

$$= V_{DD} - (2 \times 0.2)$$

$$= \boxed{2 \text{ Volts}}$$

for M₇, M₈

[15]

$$V_{DG} \leq |V_{thp}|$$

$$V_{DD} - V_b \leq |V_{thp}|$$

$$V_b \geq V_{DD} - |V_{thp}|$$

then

$$V_b = V_{DD} - |V_{thp}|$$

for $V_{SG} - V_{thp} = V_{DD}$

$$= 2.4 - 0.5$$

$$V_b = 1.9 \text{ V}$$


Problem ⑥

(16)

From the circuit sym., we will work on one half only.

Gain of half circuit = Gain of first stage * Gain of 2nd.

1st stage

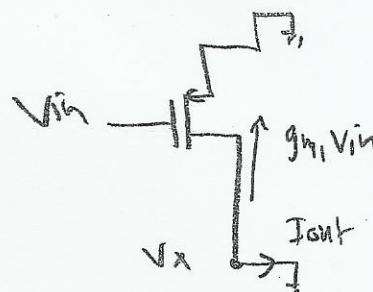


$$I_{out} = -g_m V_{in}$$

$$Gm_I = -g_m$$

$$R_{out\ I} = V_{O1} // V_{O3}$$

$$Av_I = Gm_I R_{out\ I}$$

2nd stage

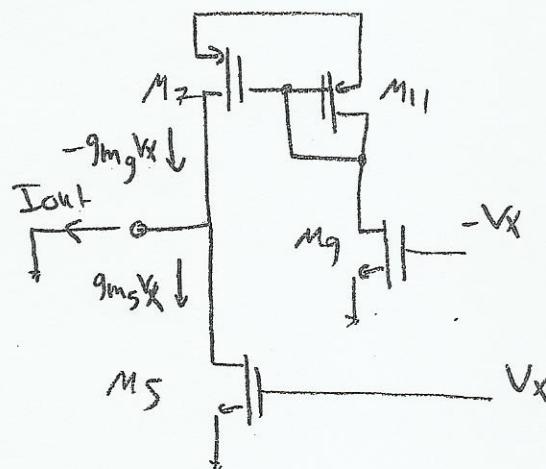

$$\begin{aligned} I_{out} &= -g_m g V_x - g_m s V_x \\ &= -(g_m g + g_m s) V_x \end{aligned}$$

for symmetry, $g_m g =$

$$I_{out} = -2g_m g V_x$$

$$Gm_{II} = -2g_m g$$

$$R_{out\ II} = V_{O7} // V_{O5}$$

then $A_{VII} = Gm_{II} R_{out\ II}$

17

then $A_V = A_{VI} A_{VII}$ (gain of half circuit)

$$A_V = 2g_m g_m (r_o / V_{O3})(V_{O7} / V_{O5})$$

8

$$A_d = -A_V \rightarrow \text{differential gain}$$