


$$I_{M1} = I_{M2}$$


SAT \leftarrow \rightarrow Triode

$$= \cancel{MnCo} \frac{W_2}{L} (V_{th} + 2V_{eff} - V_{th}) V_{eff}$$

$$W_2 = \frac{1}{4} W$$

$V_{th} + V_{eff} = V_{G1} - V_S$


 $\frac{1}{g_m} \parallel r_o = 1/g_m$

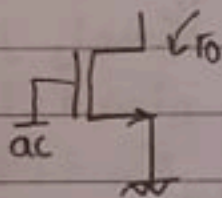

$R_{out} = r_{o2} \times g_{m1} r_{o1} + r_{o2} \parallel r_{o1}$

(B) For M_6 : $V_{DS} \geq V_{GS} - V_{th}$

$$V_{out} > 3V_{eff} + 2V_{th}$$

Hand-drawn circuit diagram of a Wilson current mirror. The circuit consists of three NMOS transistors, M_1 , M_2 , and M_3 , and two PMOS transistors, M_4 and M_6 . A reference current source I_{ref} is connected to the gates of M_5 and M_6 . M_5 is a PMOS transistor whose source is connected to the gates of M_1 and M_2 , and its drain is connected to the gates of M_3 and M_4 . M_1 and M_2 are NMOS transistors whose sources are connected to ground and whose drains are connected to the gates of M_3 and M_4 , respectively. M_3 and M_4 are PMOS transistors whose sources are connected to the gates of M_1 and M_2 , and whose drains are connected to the gates of M_5 and M_6 , respectively. The output current I_{out} is taken from the drain of M_6 . The circuit is biased with a $3V_{GS}$ signal at the gates of M_5 and M_6 , and a $2V_{GS}$ signal at the gates of M_1 and M_2 . The output voltage V_{out} is taken from the drain of M_6 . The circuit is labeled with "Small signal resistance" and V_{GS} .

diode
connected
to SAT

* assume identical transistors *

(c) Assuming random mismatches between matched transistors
Find $\frac{\Delta I_1}{I_{ref}}$

التيار M_2, M_1 لل current mirroring الذي يبعثه trans. \rightarrow يبقى في كيد دول أكثر اثنين Critical لو حصل فيه offset

$$V_{GS2} = V_{GS1} + V_{OS1}$$

$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{th})^2$$

$$I_2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} + V_{OS} - V_{th})^2$$

$$\Delta I = I_2 - I_1$$

$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) [(V_{GS} - V_{th}) + V_{OS}]^2 - (V_{GS} - V_{th})^2$$

$$+ 2 V_{OS} (V_{GS} - V_{th}) - (V_{GS} - V_{th})^2] \approx V_{OS} \lll$$

$$\Delta I \approx \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \cdot 2 V_{OS} (V_{GS} - V_{th}) \quad , \quad g_m = \frac{2 I_{ref}}{V_{eff}}$$

$$g_m$$

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}}$$

$$\Delta I \approx g_m V_{OS1}$$

$$\frac{\Delta I}{I_{ref}} = \frac{g_m V_{OS1}}{I_{ref}} = \frac{2 V_{OS1}}{V_{eff}}$$

(ال source من موصول الى ground)

due to M_4 & M_6 are degenerative so the offset in them is negligible \rightarrow

[بما أن M_4 متصلة]

على r_{o2} لا متصلة الى gnd ولا يكون فائدة ال gain الى طالع نتيجة ال V_{OS2} صغيرة أو لا تكون

PAGE _____
DATE _____

gain stage bec. the differential amplifier is just giving again

V_c لا از منبع $V_{GS} + V_{th}$
 on current source

- изготв


Hand-drawn circuit diagram for finding R_{out} . The circuit includes an op-amp with a feedback resistor R_f and a load resistor R_L . The input is a voltage source V_c . The output is connected to a load resistor R_L . The output voltage is V_x and the output current is i_x . The output resistance is R_{out} .

$$i_2 = -g_{m2} i_x r_{o1} (1 + A) = g_{m2} V_{gs}$$
$$v_x = i_x r_{o2} [1 + g_{m2} r_{o1} (1 + A)] + i_x r_{o1}$$

(D) $A = g m_3 (r_{03} // r_{05}) \rightarrow \text{of } M_3$

$$A(s) = g_{m3} (r_{o3} \parallel r_{o5} \parallel 1/s_c) \left(\frac{1}{1+s/\omega_p} \right) \left[r_{o2} + g_{m2} r_{o2} (1+A(s)) \right]$$

(4) Find A_v , R_{out} , R_{in} , G_m

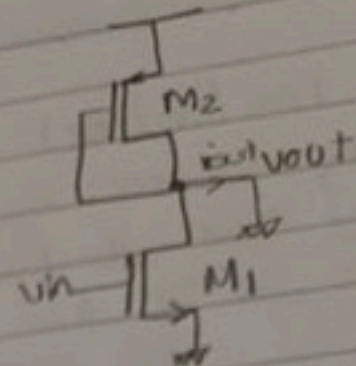


- $R_{in} = \infty$ (Source has infinite resistance)
- [Transconductance of the circuit] \rightarrow input voltage \rightarrow output current

$$R_{out} = 1/g_{m2} \parallel r_{o2} \parallel r_{o1}$$

G_m

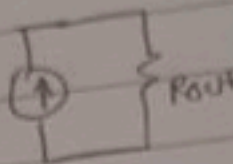قوة ابعاد الـ $o.c.t.$ \rightarrow input voltage \rightarrow output current





$$G_m = \frac{i_{out}}{v_{in}} = -\frac{g_{m1} v_{in}}{v_{in}} = -g_{m1}$$

$$A_v = G_m \cdot R_{out} = -g_{m1} \cdot (1/g_{m2} \parallel r_{o1} \parallel r_{o2})$$

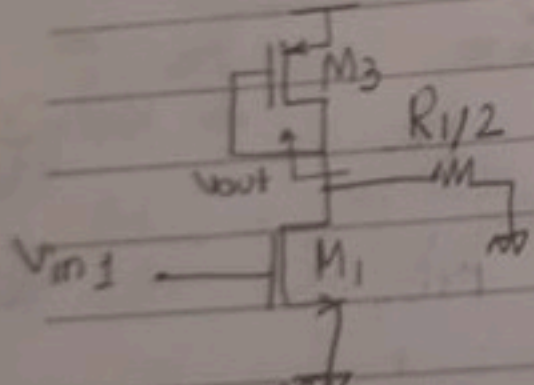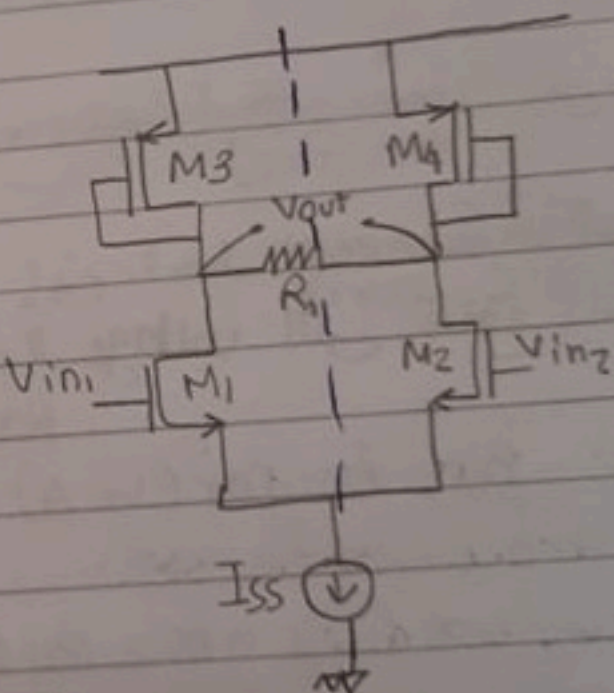
(5) Find A_v , diff.

due to the symmetry in the ckt. we can draw a half ckt.




$$A_v = -g_{m1} \left(\frac{1}{g_{m3}} \parallel r_{o3} \parallel \frac{R_1}{2} \parallel r_{o1} \right)$$

→ Saturation Conditions:

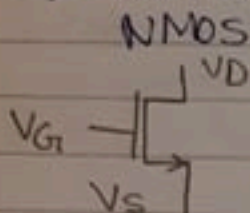


$$V_{DS} > V_{GS} - V_{th}$$

$$V_{GD} < V_{th}$$

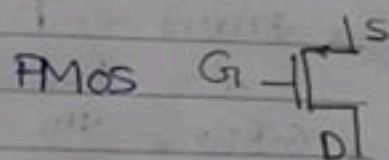

$$V_{D,max} = V_{G1} + |V_{th}|$$

$$V_{G1,min} = V_D - |V_{th}|$$

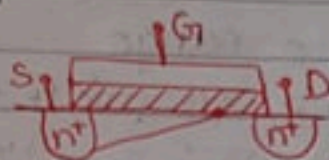


$$V_{Dmin} = V_{G1} - V_{th}$$


$$V_{G1,max} = V_D + |V_{th}|$$

يبقى هنا ال Sat معناها عدم قدرة
ال channel على تحمل كذا الاقتراف
pinchoff

→ op-amps:

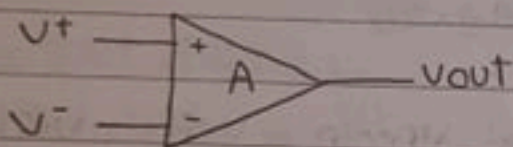

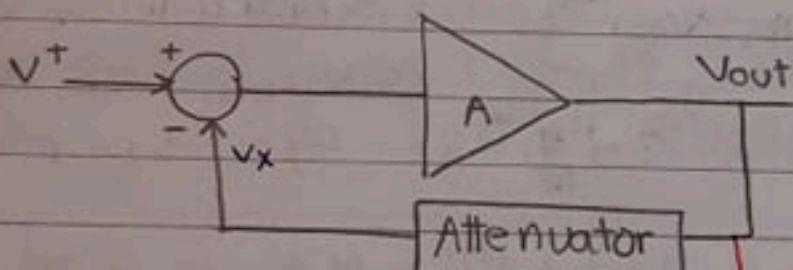
هو بسيط 2 inputs بعضو بعضوهم
على و بتظهر اهمية خال feedback loop



→ This is a high-precision amplifier

لانه يقلل الفرق بين V+ و Vx خالص


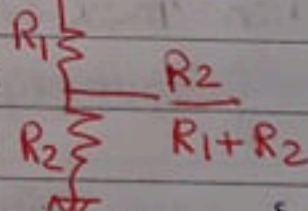
$$V_{out} = V^+ \left(1 + \frac{R_2}{R_1 + R_2} \right)$$



attenuator feedback amplifier apply → فهنا عازلة أ

← أقرب دائرة ال op-amplifier ال differential pair

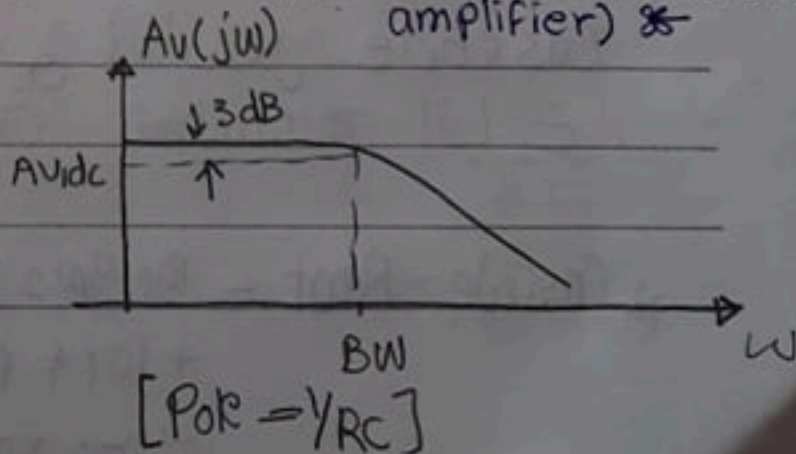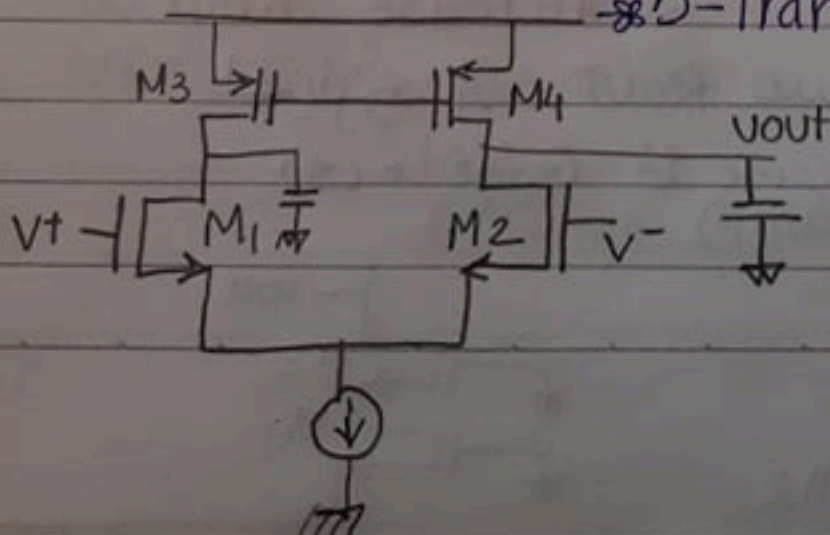→ 5-transistor OTA (operational transconductance amplifier)



at small signal analysis

$$* A_{v,dc} = -g_m (r_{o2} \parallel r_{o4}) \rightarrow \text{Is open circuit.}$$

$$* BW = \frac{1}{C_L (r_{o2} \parallel r_{o4})}$$

$$* G_{BW} = \frac{g_m}{C_L} \quad (\text{closed loop P.B.W} \propto G_{BW})$$

بجهد ال Speed تابع الدائرة

* input common mode range

$$V_{cm,min} = V_{comp,ISS} + v_{eff1} + v_{th}$$

$$V_{cm,max} = V_{DD} - V_{SG3} = V_{DD} - (v_{eff3} + v_{th3}) + v_{th1}$$

أنا خيفة أن M_1 يخرج ما ر SAT في $V_{cm,max}$ $+v_{th1}$



* output swing:

$$v_{out,max} = V_{DD} - v_{eff4} \quad (\text{خيفة لا } M_4 \text{ يخرج ما ر SAT})$$

$$v_{out,min} = V_{cm} - v_{th1} \quad (\text{خيفة } M_2 \text{ لا يخرج ما ر SAT})$$

إلى راضعني ISS شغال

Note

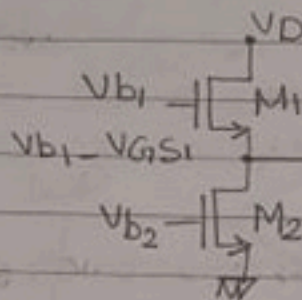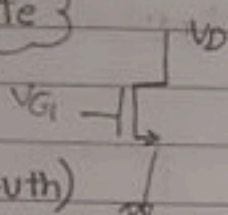

$$V_{Dmin} = v_{eff2} + v_{eff1}$$

only valid if $V_{D2} = v_{eff2}$

$$V_{Dmin} = V_{B1} - v_{th1}$$

* Slew rate:

$$SR = \left(\frac{dv_{out}}{dt} \right)_{max}$$

$$v_{out} = \frac{1}{C} \int i_{out}(+) dt, \quad i_{out} = C \frac{dv_{out}}{dt}$$


$$\left(\frac{dv_{out}}{dt} \right)_{max} = \frac{I_{out,max}}{C} = \frac{I_{SS}}{C_L}$$

أنا عايزة أزود ال gain تابع الدائرة إلى فانت لى سبب من

$$\% \text{ gain} = G_m R_{out} \quad \text{increase } R_{out}$$

أنا أزود ال R_{out} عن طريق أنا زعل Cascode
 زي ما هتفوق (telescopic OP-amp) كالمشكلة الباية

$$* \text{Cascode } R_{out} = r_{o1} g_{m2} r_{o2} + r_{o1} + r_{o2} \approx r_{o1} r_{o2} g_{m2}$$

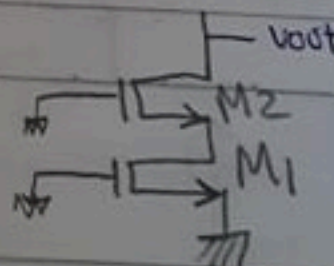

Sheet 2:
problem 1 :-

$$(1) A_{v,dc} = \frac{-g_{m1}(R_{up} \parallel R_{down})}{g_{m1,2}(r_{o8} r_{o6} g_{m6} \parallel r_{o2} r_{o4} g_{m4})}$$

∞ all r_{o} g_m are equal

$$\& A_{v,dc} \approx -g_{m1} (g_{mro})^2$$

gain $\propto \frac{1}{\sqrt{I_{SS}}} \propto \frac{1}{\sqrt{C_L}}$

$$(2) G_{BW} = \frac{g_{m1}}{C_L}$$

$$BW = \frac{1}{R_{out} C_L}$$

$$(3) \text{Slew rate} = \frac{I_{SS}}{C_L}$$

(4) output Swing:

$$V_{out,max} = V_{b2} + |V_{th6}|$$

$$V_{out,min} = V_{b1} - V_{th4}$$

for max output swing ($V_{b2} \uparrow \uparrow$, $V_{b1} \downarrow \downarrow$)

$$V_{b2}|_{max} = V_{DD} - V_{eff7} - (V_{eff6} + V_{th6})$$

$$V_{b1}|_{min} = V_{CM} - V_{th1} + V_{GS3}$$

$$\rightarrow (V_{eff3} + V_{th3})$$

at the assumption of $V_{CM} = V_{comp} + V_{eff} + V_{th1}$

$$\& \text{max. o/p swing} = V_{max} - V_{min} = V_{DD} - (4V_{eff} + V_{comp})$$


(5) Input CM R: ←

$$V_{cm,min} = V_{comp,ISS} + V_{eff1} + V_{th1}$$

$$V_{cm,max} = V_{DD} + V_{th} = (V_{b1} - V_{GS3}) + V_{th1}$$

$$\frac{I_{SS}}{C_L} \neq SR \quad \text{السرعة القصوى} \neq \frac{I_{SS}}{C_L}$$

Telescopic op-amp

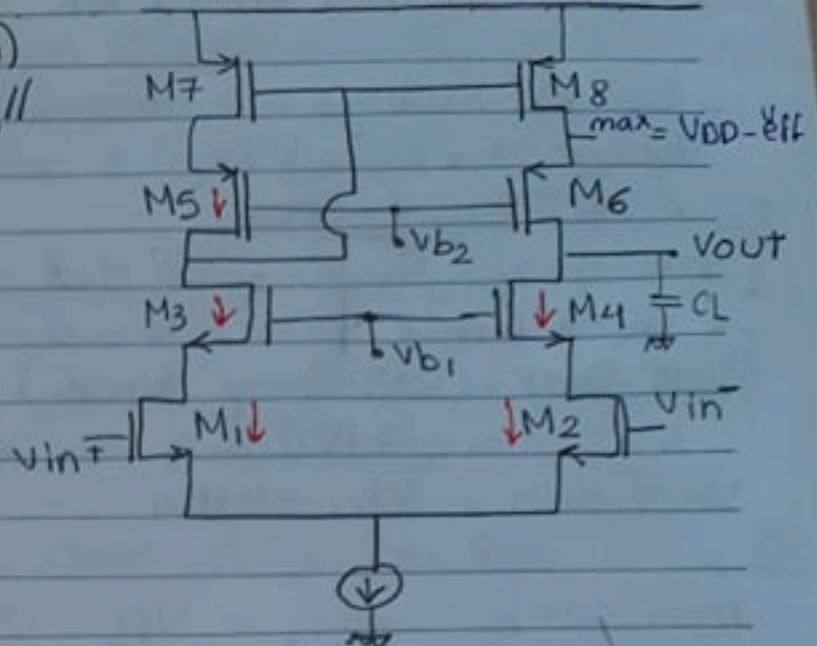

Current mirror ∞
Symmetry في الـ node

مابين الناحيتين

- Same $A_{v,dc}$, GBW , BR

- out put swing:

$$V_{out, max} = V_{G1} + |V_{th6}|$$

تجارب الـ M6 أو M8

يُخْرِجُوا مَا فِي سَاتِ

$$V_{out, max} = (V_{DD} - V_{SG7} - V_{SG5}) + |V_{th}6|$$

$$V_{out, max} = (V_{DD} - V_{SG7} - V_{SG5}) + |V_{th}16|$$

$$V_{out, \min} = V_{b_1} - V_{th4}$$

$$\text{max out put swing} = V_{DD} - (3V_{eff} + V_{SG1} + V_{comp, I_{SS}})$$

$$V_{b \text{ min}} = V_{eff3} + V_{th3} + V_{eff1} + V_{comp \text{ ISS}}$$

$$V_{G_{max}} = V_{DD} - V_{SG17} - V_{eff6}$$

$$\Delta V_{out, max} - V_{out, min} = V_{DD} - V_{SG17} - V_{eff} + V_{th6}$$

~~$$(V_{eff} + V_{th3} + V_{eff} + V_{comp, Iss}) + V_{th4}$$~~

$$= V_{DD} - (3V_{eff} + V_{SG17} + V_{comp, ISS}) + v_{th6}$$