


(1)

Date:

Subject:

Operational Amplifiers

Problem 1:

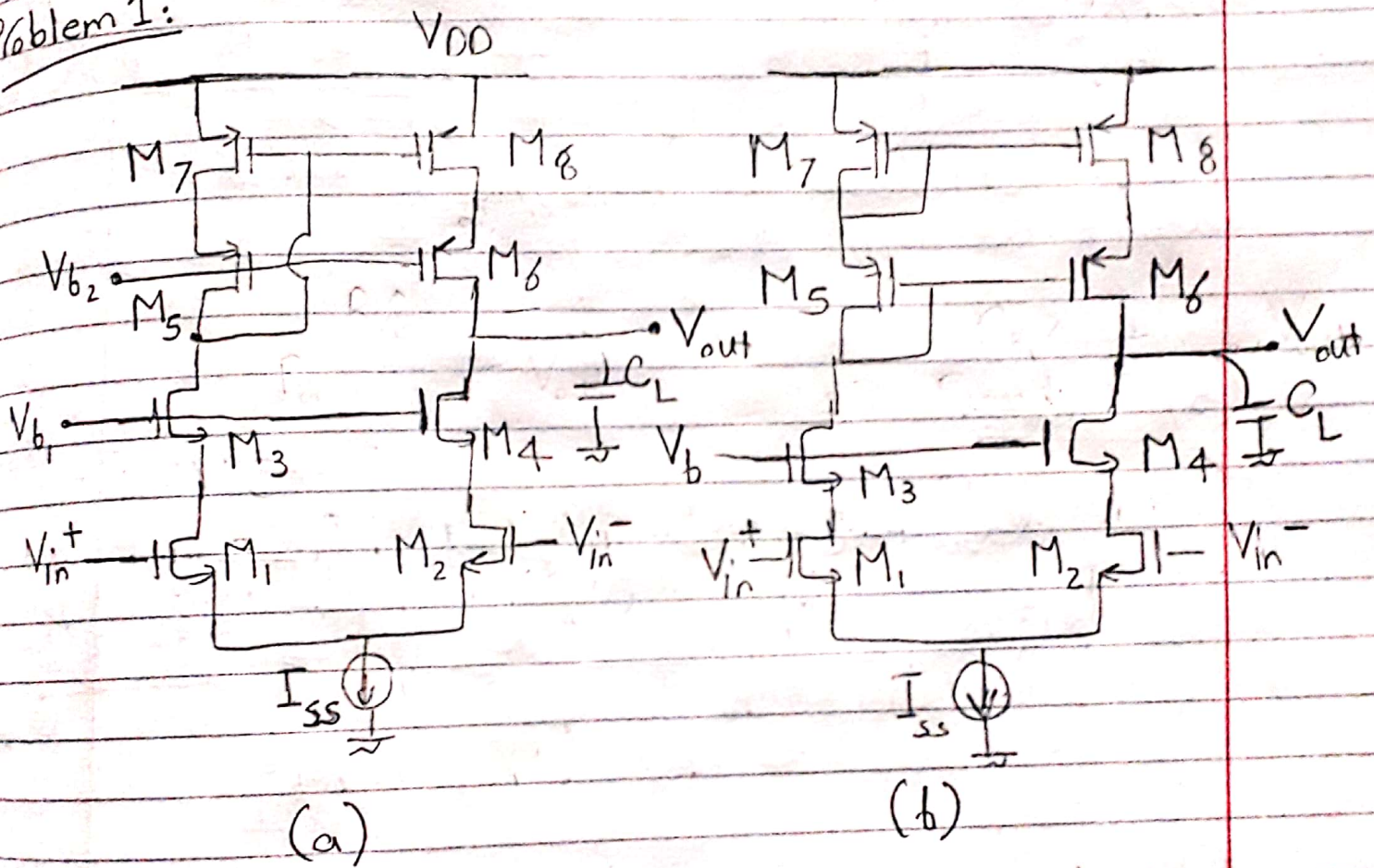

Compare between the two operational amplifier circuits in terms of:

① DC gain: Both have the same DC gain

$$G_m = g_{m1}$$

$$R_{out} \approx (g_{m6} r_{o6} r_{o8} // g_{m4} r_{o4} r_{o2})$$

$$\therefore A_v \approx -g_{m1} (g_{m6} r_{o6} r_{o8} // g_{m4} r_{o4} r_{o2})$$

(2)

② GBW (assume a load Capacitance C_L):

dominant Pole \rightarrow B.W. = $\frac{1}{R_{out} C_L}$

\therefore GBW = $A_v \cdot \text{B.W.} = \frac{g_{m1}}{C_L}$ (for both)

③ Slew rate:

If $V_{in, \text{differential}}$ is large enough, current (I_{ss}) will be steered in one branch. Therefore, the whole biasing current (I_{ss}) will be pushed into or pulled from C_L

\therefore SR = $\pm \frac{I_{ss}}{C_L}$ (for both)

④ Maximum available output swing:

$M_6 \text{ sat}$ Circuit (a)

* $V_{out, \max} = V_{b2} + V_{th,6}$

* $V_{out, \min} = V_{b1} - V_{th,4}$

* o/p swing = $V_{out, \max} - V_{out, \min}$

* To maximize o/p swing:

Choose: $V_{b1} = V_{GS3} + V_{eff,1} + V_{Comp, I_{ss}}$

$V_{b2} = V_{DD} - V_{eff,7} - V_{SG5}$

$V_{in, CM} = V_{GS1} + V_{Comp, I_{ss}}$

Hence, o/p swing_{max} = $V_{DD} - (\sum V_{eff} + V_{Comp, I_{ss}})$

Circuit (b)

* $V_{out, \max} = V_{DD} - V_{SG7} - V_{eff,6}$

* $V_{out, \min} = V_b - V_{th,4}$

* o/p swing = $V_{out, \max} - V_{out, \min}$

* To maximize o/p swing:

Choose: $V_b = V_{GS3} + V_{eff,1} + V_{Comp, I_{ss}}$

$V_{in, CM} = V_{GS1} + V_{Comp, I_{ss}}$

Hence, o/p swing_{max} = $V_{DD} - (V_{SG7} + 3V_{eff} + V_{Comp, I_{ss}})$

⑤ Input Common mode range (assume $V_b = V_{b1} = V_{th} + 4V_{eff}$)

Assuming equal V_{eff} for all transistors


$$\left. \begin{aligned} V_{in,CM,min} &= V_{eff} + V_{th1} + V_{Comp,Iss} \\ V_{in,CM,max} &= 3V_{eff} + V_{th1} \end{aligned} \right\} \text{ for both}$$

⑥ Noise & offset:

$$V_{n,in}^2 = 2 * \left[\frac{4KT\gamma}{g_{m1}} + \frac{4KT\gamma g_{m7}}{g_{m1}^2} \right] = \frac{8KT\gamma}{g_{m1}} \left[1 + \frac{g_{m7}}{g_{m1}} \right]$$

$$V_{os,in}^2 = V_{os,1-2}^2 + V_{os,7-8}^2 * \frac{g_{m7}^2}{g_{m1}^2}$$

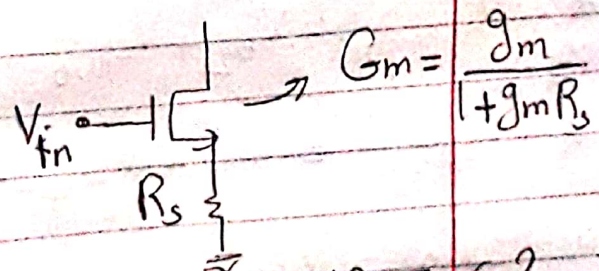* The noise and offset of CasCode devices can be neglected because their overall transconductance is very small as they are degenerated



⑦ Why will the transfer fn. $A(s)$ have LHP Zeros?

* Because there are two paths from the input to output with different frequency dependence


Analysis can be found in Lec slides

Problem(2):

Study the stability of the self regulated current source.

Solution

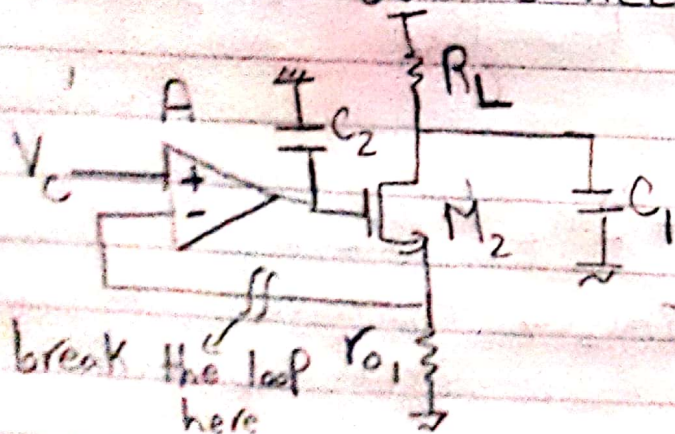- * In order to judge the stability, we'll calculate the loop gain transfer function by breaking the loop, injecting a signal, and calculating the gain it experiences through the loop
- * Stability can then be determined from the Poles and Zeros locations
- * For reasonable stability, Phase margin of about 60° is needed at the unity-gain freq.




(5)

Date.....

$$A(s) = g_{m4}(r_{o4} // r_{o6} // \frac{1}{sC_2})$$
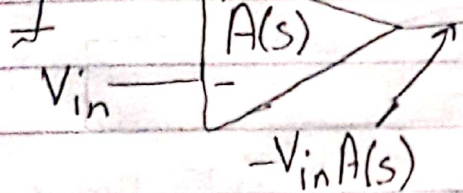
$$= \frac{g_{m4}(r_{o4} // r_{o6})}{1 + sC_2(r_{o4} // r_{o6})}$$



$$-g_{m2}(V_{in} A(s) + V_{out}) - \left(\frac{V_{out} R_L}{r_{o1} r_{o2}} + \frac{V_{out}}{r_{o2}} \right)$$

KCL @ V_{out} :

$$-g_{m2}(V_{in} A(s) + V_{out}) - \frac{V_{out}}{r_{o2}} \left(\frac{R_L/r_{o1}}{1 + sC_1 R_L} + 1 \right) = \frac{V_{out}}{r_{o1}}$$

$$V_{out} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_{m2} + \frac{R_L/r_{o1} r_{o2}}{1 + sC_1 R_L} \right) = -g_{m2} A(s) V_{in}$$

Can be neglected

$$\therefore \text{Loop gain}(s) = \frac{V_{out}(s)}{V_{in}} = \frac{-g_{m2} A(s)}{g_{m2} + \frac{R_L/r_{o1} r_{o2}}{1 + sC_1 R_L}}$$

$$= \frac{-g_{m2} g_{m4} (r_{o4} // r_{o6}) / (1 + sC_2 (r_{o4} // r_{o6}))}{g_{m2} + \frac{R_L/r_{o1} r_{o2}}{1 + sC_1 R_L}}$$

$$= \frac{-g_{m2} g_{m4} (r_{o4} // r_{o6}) (1 + sC_1 R_L)}{\left(g_{m2} + \frac{R_L}{r_{o1} r_{o2}} + sC_1 g_{m2} R_L \right) (1 + sC_2 (r_{o4} // r_{o6}))}$$

6

Date.....

Subject.....

$$= \frac{-g_{m_2} g_{m_4} (r_{o4} // r_{o6})}{g_{m_2} + \frac{R_L}{r_{o1} r_{o2}}} (1 + s C_1 R_L)$$

$$\frac{(1 + s C_1 g_{m_2} R_L) (1 + s C_2 (r_{o4} // r_{o6}))}{g_{m_2} + \frac{R_L}{r_{o1} r_{o2}}}$$

In general, there are 2 Poles + LHP Zero

if $g_{m_2} \gg \frac{R_L}{r_{o1} r_{o2}} \rightarrow g_{m_2} r_{o1} r_{o2} \gg R_L$

$\therefore \text{Loop gain}(s) \approx \frac{-g_{m_4} (r_{o4} // r_{o6})}{1 + s C_2 (r_{o4} // r_{o6})}$

STOTA DC gain * Source follower DC gain
 (= 1 because we assumed $\frac{1}{r_{o1}} + \frac{1}{r_{o2}} \ll g_{m_2}$)
 just 1 Pole at the STOTA output

→ The loop will be UnConditionally stable
 (Note that we haven't considered the Parasitic Cap. at the source of M_2)