


Problem 13.2 $\frac{Y}{X}(s) = \frac{H(s)}{1 + H(s)[K(s) + G(s)]}$

For this system to oscillate $-ve \text{ FB} \rightarrow +ve \text{ FB}$

$1 + H(s)[K(s) + G(s)] = 0$ Let $K(s) + G(s) = N(s)$

$H(s)N(s) = -1$ $|H(j\omega_{osc})| \cdot |N(j\omega_{osc})| \geq 1$

$\angle H(j\omega_{osc}) + \angle N(j\omega_{osc}) = 180^\circ$

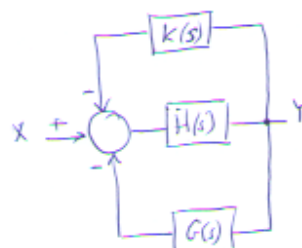

Problem 13.6

Loop Gain = $LG = \frac{V_{out}}{V_N} = \frac{V_{out}}{V_X} \cdot \frac{V_X}{V_N}$

$\frac{V_X}{V_N} = -g_{m2} [R_D \parallel \frac{1}{s(2C_B)}] = \frac{-g_{m2} R_D}{1 + sR_D(2C_B)}$

$= -\frac{A_0}{1 + \frac{s}{\omega_{p1}}}$ $A_0 = \text{DC gain} = g_{m2} R_D$
 $\omega_{p1} = \frac{1}{R_X C_X}$ $R_X = R_D$ $C_X = 2C_B$

$\frac{V_{out}}{V_X} = \frac{g_{m4} Z_L}{1 + g_{m4} Z_L} = \frac{g_{m4} \frac{1}{sC_L}}{1 + g_{m4} \frac{1}{sC_L}} = \frac{g_{m4}}{g_{m4} + sC_L} = \frac{1}{1 + \frac{sC_L}{g_{m4}}}$

$= \frac{1}{1 + \frac{s}{\omega_{p2}}}$ $1 = \text{DC gain (source follower)}$ $R_{out} = \frac{1}{g_{m4}}$ $C_{out} = C_L$
 $\omega_{p2} = \frac{1}{R_{out} C_{out}}$



$LG = -\frac{A_0}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})} = -H(s)$

For the system to oscillate

$\angle H(j\omega) = -180^\circ$ happens at $\omega = \infty$
 $|H(j\omega)| \geq 1$ where $|H(j\omega)| \approx 0 (< 1)$

Thus the system cannot oscillate

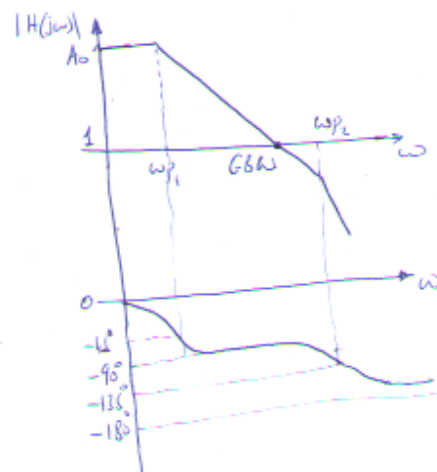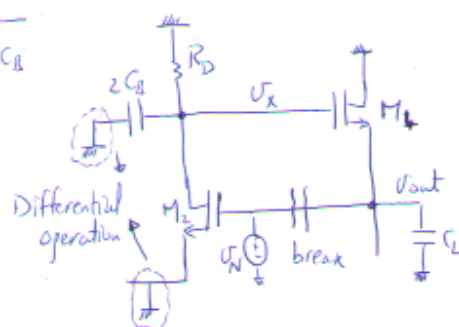However we need to calculate & design for good PM ($\geq 60^\circ$)



$$\omega_{p1} = \frac{1}{R_D(2C_S)} = \omega_d = \frac{1}{10k \times 1p} = 100 \text{ Mrad/sec (dominant pole)}$$

$$\omega_{p2} = \frac{g_{m4}}{C_L} = \omega_{nd} = \frac{10ms}{2p} = 5000 \text{ Mrad/sec (non-dominant pole)}$$

$$GBW = A_0 \cdot \omega_d = \frac{g_{m2}}{2C_S} = \frac{1n}{1p} = 1000 \text{ Mrad/sec} = 1 \text{ Grad/sec}$$

$$\angle H(j\omega) = -\tan^{-1}\left(\frac{GBW}{\omega_{p1}}\right) - \tan^{-1}\left(\frac{GBW}{\omega_{p2}}\right) = -90^\circ - \tan^{-1}\left(\frac{1G}{5G}\right) = -101^\circ$$

$$PM = 180 - 101 = 79^\circ$$

$$\text{For } PM > 60^\circ \quad \omega_{nd} > 2 GBW \quad \frac{g_{m4}}{C_L} > 2 \text{ Grad/sec} \quad C_L < 5pF$$

- * In this problem, ω_d is fixed and ω_{nd} is at the output (C_L)
 This large C_L would result in small ω_{nd} (GBW is fixed depend on C_S) and bad PM

Problem 13.7


A 3rd pole is created in the loop gain $\underline{H}(s)$

$$\omega_{p3} \approx \frac{1}{R_S C_{GS}} = \frac{1}{10k \times 100f} = 1 \text{ Grad/sec}$$

$$\angle H(j\omega) = -\tan^{-1}\left(\frac{GBW}{\omega_{p1}}\right) - \tan^{-1}\left(\frac{GBW}{\omega_{p2}}\right) - \tan^{-1}\left(\frac{GBW}{\omega_{p3}}\right) \\ = -90 - 101 - \tan^{-1}\left(\frac{1G}{1G}\right) = -146^\circ$$

$$PM = 180 - 146 = 34^\circ \text{ (bad PM)}$$

PM reduces for increased number of poles

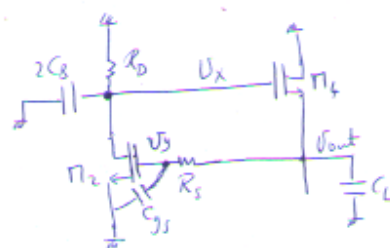

$$R_S + \frac{1}{g_{m4}} \approx R_S$$

C_L is considered open when calculating Resistance to $\frac{1}{g_{m4}}$ of C_{GS} at node U_X


Problem 13.8 & 13.9

$$H_{\text{unit}} = \frac{V_X}{V_Z} = - \frac{g_m R_D}{(1 + \frac{s}{\omega_p})}$$

$$A_0 = g_m R_D$$

$$\omega_p = \frac{1}{R_D C_D}$$
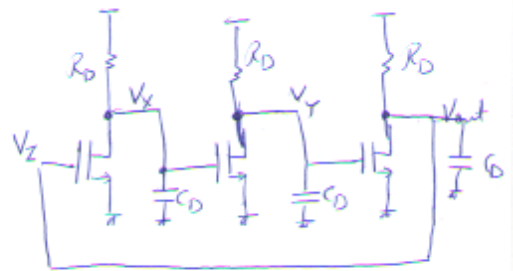
$$H(s) = H_{\text{unit}}^3 = \left(\frac{-A_0}{1 + \frac{s}{\omega_p}} \right)^3 = - \frac{A_0^3}{(1 + \frac{s}{\omega_p})^3}$$



Edge of Oscillation $H(s) = 1$

$$\frac{-A_0^3}{(1 + s R_D C_D)^3} = 1 \quad + A_0^3 + 1 + 3s R_D C_D + 3(s R_D C_D)^2 + (s R_D C_D)^3 = 0$$

put $s = j\omega_{osc}$

$$\begin{aligned} \text{Real} &= 1 + A_0^3 - 3\omega_{osc}^2 (R_D C_D)^2 = 0 \Rightarrow A_0 = 2 \text{ (min gain)} \\ \text{Imaginary} &= 3\omega_{osc} R_D C_D - \omega_{osc}^3 R_D^3 C_D^3 = 0 \Rightarrow \omega_{osc} = \frac{\sqrt{3}}{R_D C_D} \end{aligned}$$

start-up condition $A_0 \geq 2 \quad g_m R_D \geq 2$

Oscillation freq $\omega_{osc} = \frac{\sqrt{3}}{R_D C_D}$

$R_D \times 2 \quad A_0 \times 2 \quad (\text{better startup}) \quad \frac{\omega_{osc}}{2}$
 $C_D \times 2 \quad A_0 \text{ same} \quad (\text{no change in startup}) \quad \frac{\omega_{osc}}{2}$



Problem 13.12 $H(s) = H_{\text{unit}}^5 = - \frac{A_0^5}{[1 + \frac{s}{\omega_0}]^5} \quad A_0 = g_m R_D \text{ \& } \omega_0 = \frac{1}{R_D C_D}$

$$|H(j\omega_{osc})| = -180 - 5 \tan^{-1}\left(\frac{\omega_{osc}}{\omega_0}\right) = -360^\circ \quad (\text{no other multiple of } 360^\circ)$$

$$\tan^{-1}\left(\frac{\omega_{osc}}{\omega_0}\right) = \frac{180^\circ}{5} = 36^\circ \Rightarrow \omega_{osc} = 0.73 \omega_0$$

startup condition $|H(j\omega_{osc})| \geq 1 \quad \frac{A_0^5}{[1 + (\frac{\omega_{osc}}{\omega_0})^2]^5} \geq 1 \Rightarrow A_0 \geq 1.53$

Problem 13.16

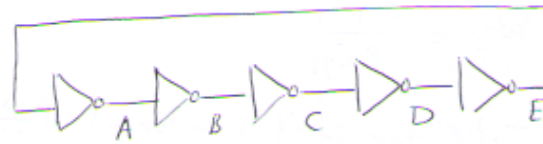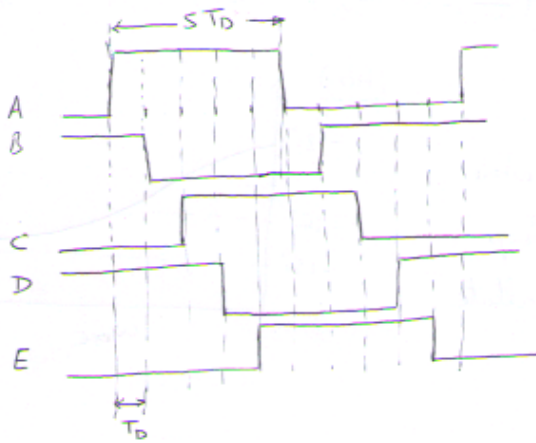

Assume delay of each inverter is T_D

$$T_{\text{period}} = 10 T_D = 2 * \# \text{stages} * T_D$$

$$f_{\text{osc}} = \frac{1}{T_{\text{period}}}$$