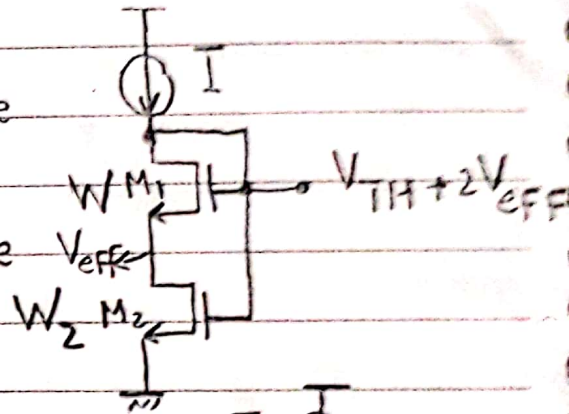


(1)

Problem Set: Advanced Current Mirrors

Problem 1:


The circuit shown is used to bias a low-voltage (high-swing) Cascode current mirror. Show that $W_2 = \frac{1}{3}W$ to generate the required bias voltage $V_{TH} + 2V_{eff}$



Solution

→ M_2 is in triode region

sat. ← $I_{M1} = I_{M2}$ → triode

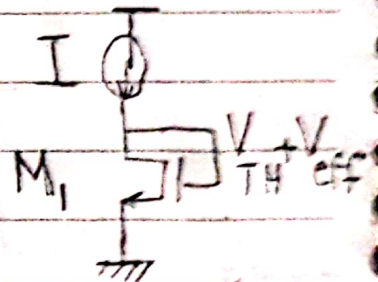


$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{TH} + V_{eff} - V_{TH})^2 = \mu_n C_{ox} \frac{W_2}{L} \left[(V_{TH} + 2V_{eff} - V_{TH}) V_{eff} - \frac{V_{eff}^2}{2} \right]$$

$$\frac{1}{2} W V_{eff}^2 = \frac{3}{2} W_2 V_{eff}^2$$

$$W_2 = \frac{1}{3} W$$

Problem 2:

Assuming all transistors are identical

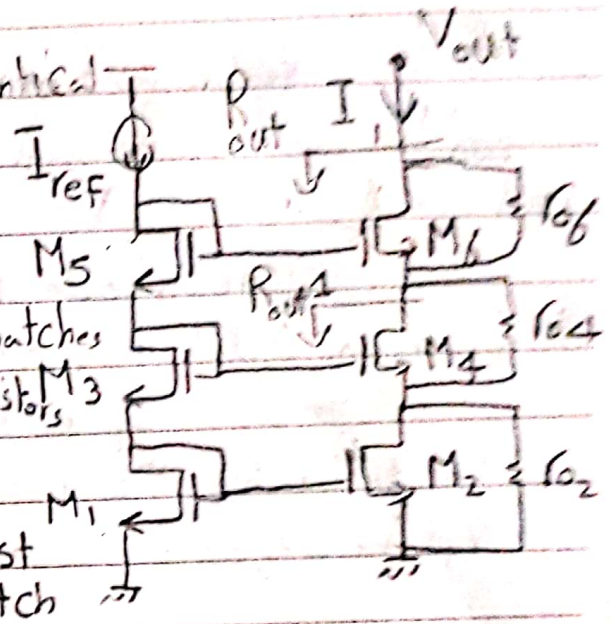Find: A. R_{out} B. Compliance Voltage
of the current source M_5 C. Assuming random mismatches
between matched transistors M_3
(V_{os}) Find $\frac{\Delta I_1}{I_{ref}}$ (Consider only the most
dominant mismatch)Solution

$$\boxed{A} \quad R_{out1} = g_{m4} r_{o4} r_{o2} + r_{o2} + r_{o4}$$

$$R_{out} = g_{m6} r_{o6} R_{out1} + R_{out1} + r_{o6}$$

$$\approx g_{m6} r_{o6} g_{m4} r_{o4} r_{o2}$$

$$\boxed{B} \quad V_{Comp.} = 3V_{eff} + 3V_{Th} - V_{Th} = 3V_{eff} + 2V_{Th}$$

 \boxed{C} Assuming V_{os1} mismatch between M_1 & M_2

$$I_{ref} = \frac{K_n}{2} (V_{GS1} - V_{Th})^2$$

$$I_1 = \frac{K_n}{2} (V_{GS1} + V_{os1} - V_{Th})^2$$

$$= \frac{K_n}{2} \left[(V_{GS1} - V_{Th})^2 + 2V_{os1}V_{eff} + V_{os1}^2 \right]$$

$$I_1 = I_{ref} + K_n V_{eff} V_{os1}$$

$$I_1 = I_{ref} + g_m V_{os1}$$

$$\frac{I_1 - I_{ref}}{I_{ref}} = \frac{g_m V_{os1}}{I_{ref}} = \frac{2I_{ref}/V_{eff} V_{os1}}{I_{ref}}$$

$$= \frac{2V_{os1}}{V_{eff}}$$


In general

$$\Delta I_{total} = \sqrt{(\Delta I_1)^2 + (\Delta I_2)^2 + (\Delta I_3)^2}$$

(3)

PAGE
DATEProblem 3:

In the shown circuit
(Self regulated current source)

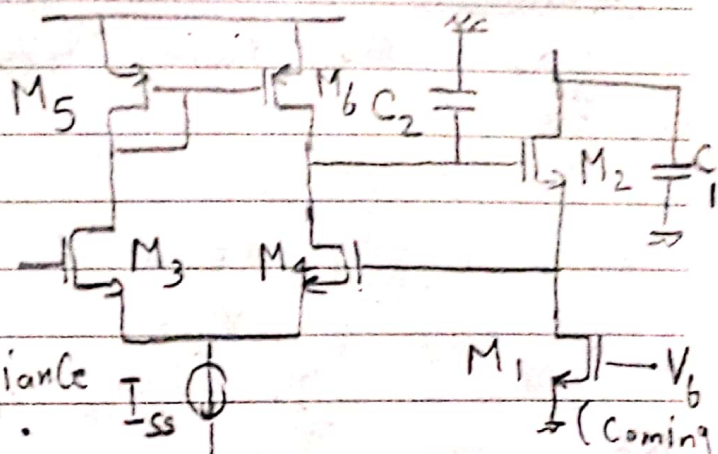Find 1. R_{out} @ DC2. Compliance Voltage V_C
of the current source3. V_C for optimum Compliance4. $Z_{out}(F)$ 

Assuming ideal I_{SS} (Can accept -ve Voltage on upper terminal)
Solution


$$2. V_{Comp.} = V_C + V_{eff2}$$

$$3. \text{For optimum Compliance, } V_C = V_{eff1}$$

$$\therefore V_{Comp.} = V_{eff1} + V_{eff2}$$

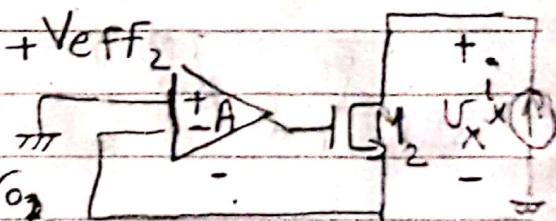1.

$$V_X = i_X r_{o1} + i_X (1 + g_{m2} r_{o1} (1 + A)) r_{o2}$$



$$R_{out} = \frac{V_X}{i_X} = r_{o1} + r_{o2} + g_{m2} r_{o2} r_{o1} (1 + A)$$


$$R_{out} \approx g_{m2} r_{o2} r_{o1} (1 + A)$$

$$A = g_{m3} (r_{o3} \parallel r_{o5}) - g_{m2} i_X r_{o1} (1 + A)$$

$$4. A(s) = g_{m3} \left(\frac{1}{sC_2} \parallel r_{o3} \parallel r_{o5} \right) - A i_X r_{o1}$$

$$= g_{m3} \cdot \frac{(r_{o3} \parallel r_{o5}) \cdot \frac{1}{sC_2}}{(r_{o3} \parallel r_{o5}) + \frac{1}{sC_2}}$$
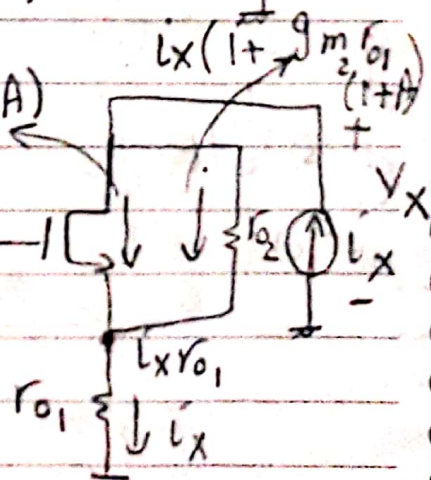
$$= g_{m3} \cdot (r_{o3} \parallel r_{o5}) \cdot \frac{1}{1 + sC_2(r_{o3} \parallel r_{o5})}$$



$$Z_{out}(s) \approx \left[g_{m2} r_{o2} r_{o1} (1 + A(s)) \right] \parallel \frac{1}{sC_2}$$

(4)


PAGE
DATE

Problem (4):

For the Wilson Current mirror shown:

- 1) Find an expression for $V_{Compliance}$ and R_{out}
- 2) Does the current mirror suffer from systematic offset? Explain

Solution

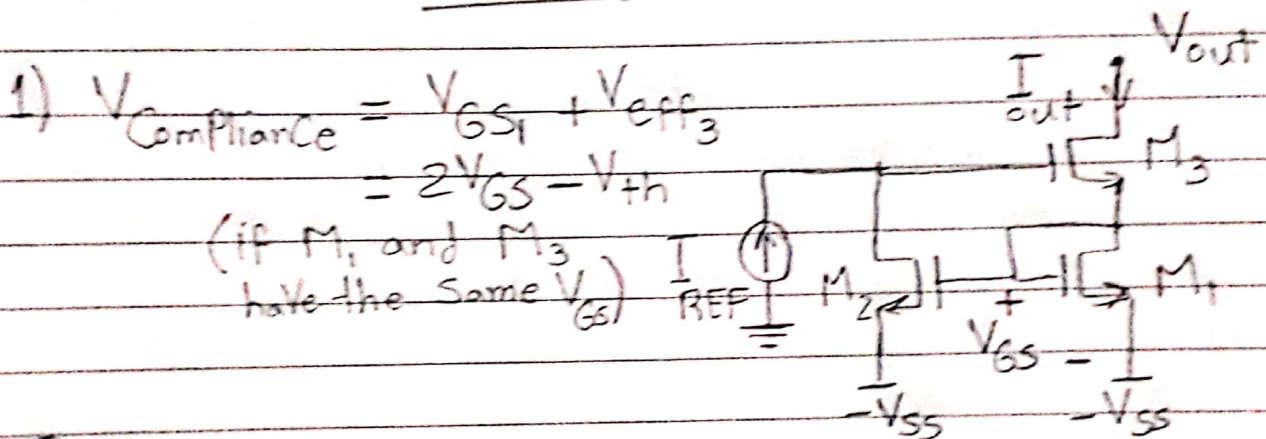

R_{out} :

$$V_y = \frac{i_x}{g_{m1}}$$

$$V_z = -g_{m2} r_{o2} V_y$$

$$= -\frac{g_{m2} r_{o2}}{g_{m1}} i_x$$

$$V_x = V_y + [i_x - g_{m3}(V_z - V_y)] r_{o3}$$

$$= \frac{i_x}{g_{m1}} + \left[1 + \frac{g_{m3}}{g_{m1}} (g_{m2} r_{o2} + 1) \right] i_x r_{o3}$$

$$R_{out} = \frac{V_x}{i_x} \approx \frac{g_{m3}}{g_{m1}} g_{m2} r_{o2} r_{o3}$$

- 2) Yes, $V_{DS1} \neq V_{DS2}$.

$$V_{DS1} = V_{GS1}$$

$$V_{DS2} = V_{GS1} + V_{GS3}$$

$$I_{out} = \frac{W_1}{W_2} I_{REF} \frac{(1 + \lambda V_{GS1})}{[1 + \lambda(V_{GS1} + V_{GS3})]}$$